

Webinar:

MMC- Technologies

Presenters: Juan Carlos Garcia and Farid Mosallat

February 26 - 2015

Table of contents


1. Modular multi-level converters
2. dq decoupled vector current control
3. Half and H-bridge converters
4. Detailed equivalent models of MMC valves
5. Simulation of a two-terminal system
6. Simulation of a dc-fault and re-start process (half- and H-bridge MMCs)
7. Setup of a three-terminal system (on-line demonstration – if time allows)
8. Questions

If you have questions during the Webinar

- Please e-mail PSCAD Support at

support@pscad.com

Grid-connected VSC: Operation principle

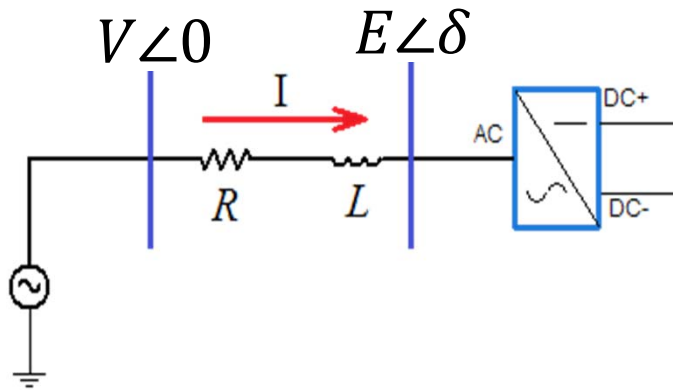


Neglecting R:

$$I = \frac{V\angle 0 - E\angle \delta}{jX_L}$$


$$S = VI^* \Rightarrow$$

$$\begin{cases} P = -\frac{EV}{X_L} \sin(\delta) \\ Q = \frac{V^2 - EV \cos(\delta)}{X_L} \end{cases}$$

Supplying P:

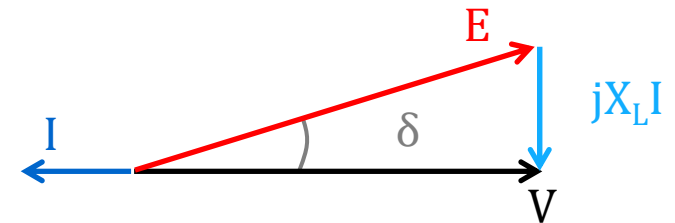


Absorbing P:

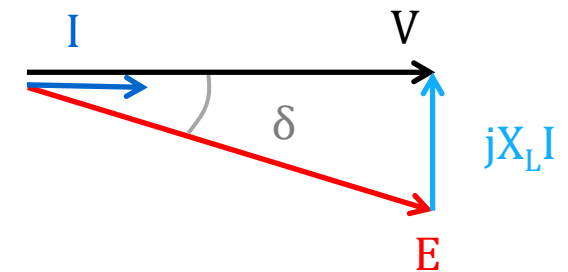

Supplying Q:





Absorbing Q:

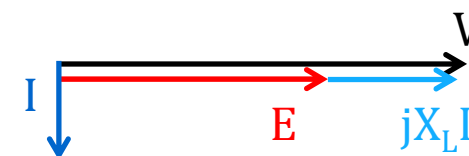


Phase Locked Loop (PLL)

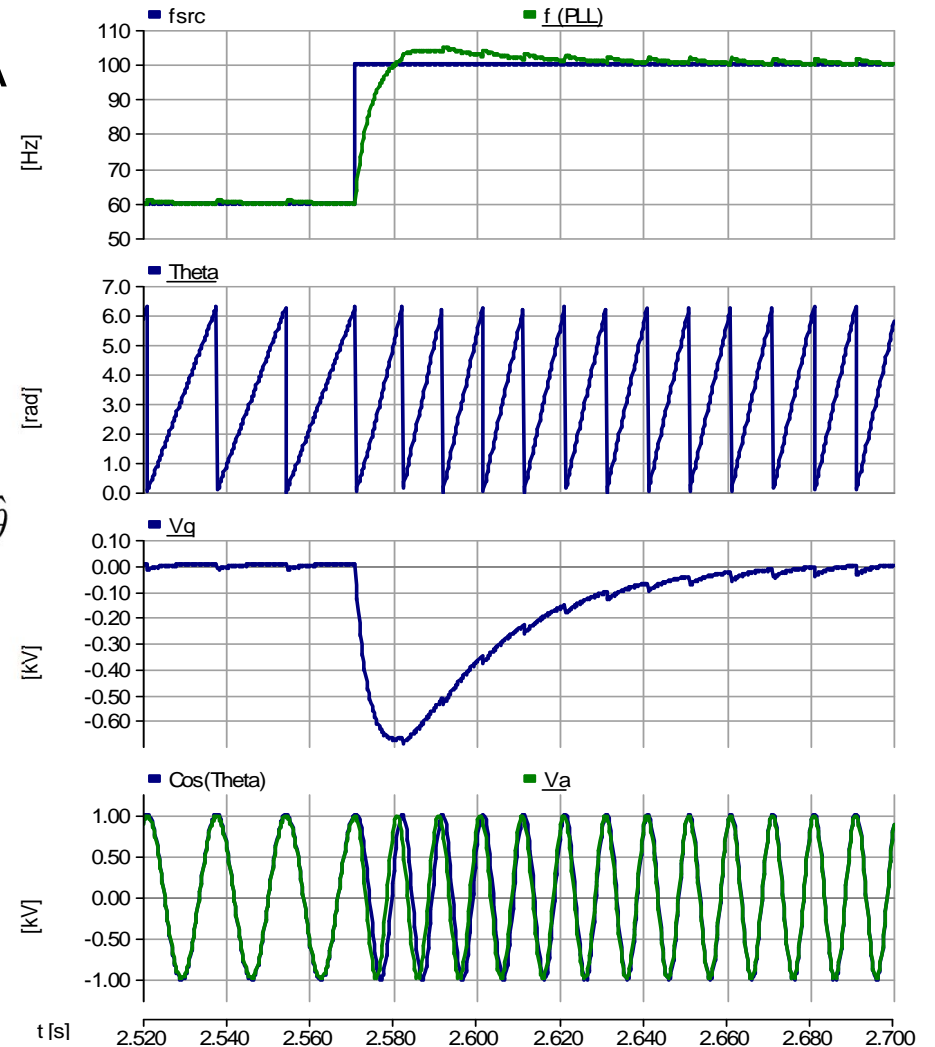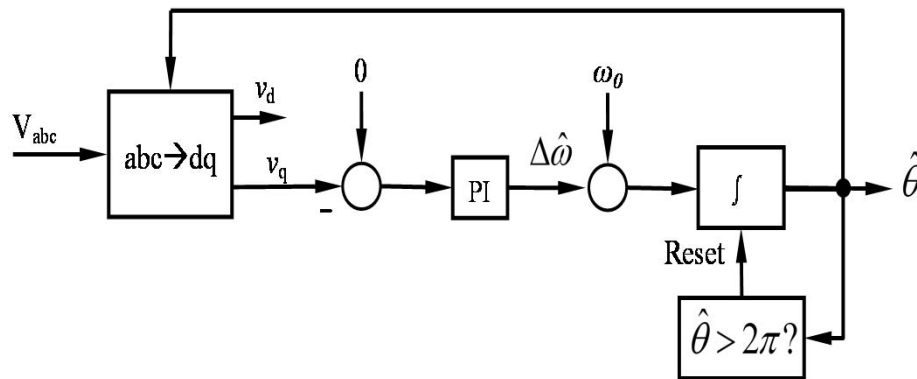Extracting the phase angle of phase-A voltage




Control modes for grid-connected operation

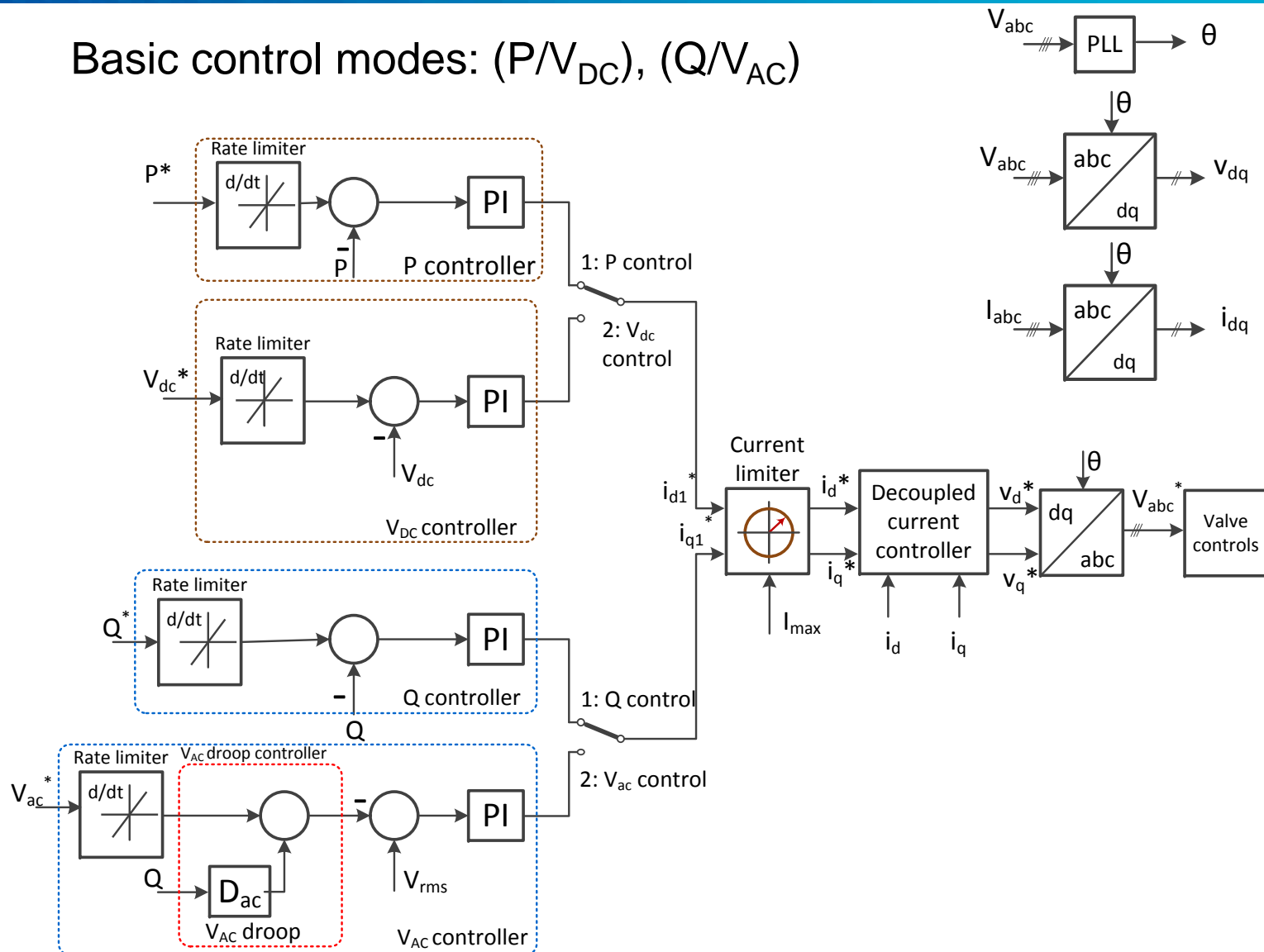Basic control modes: (P/ V_{DC}), (Q/ V_{AC})





Decoupled current control strategy


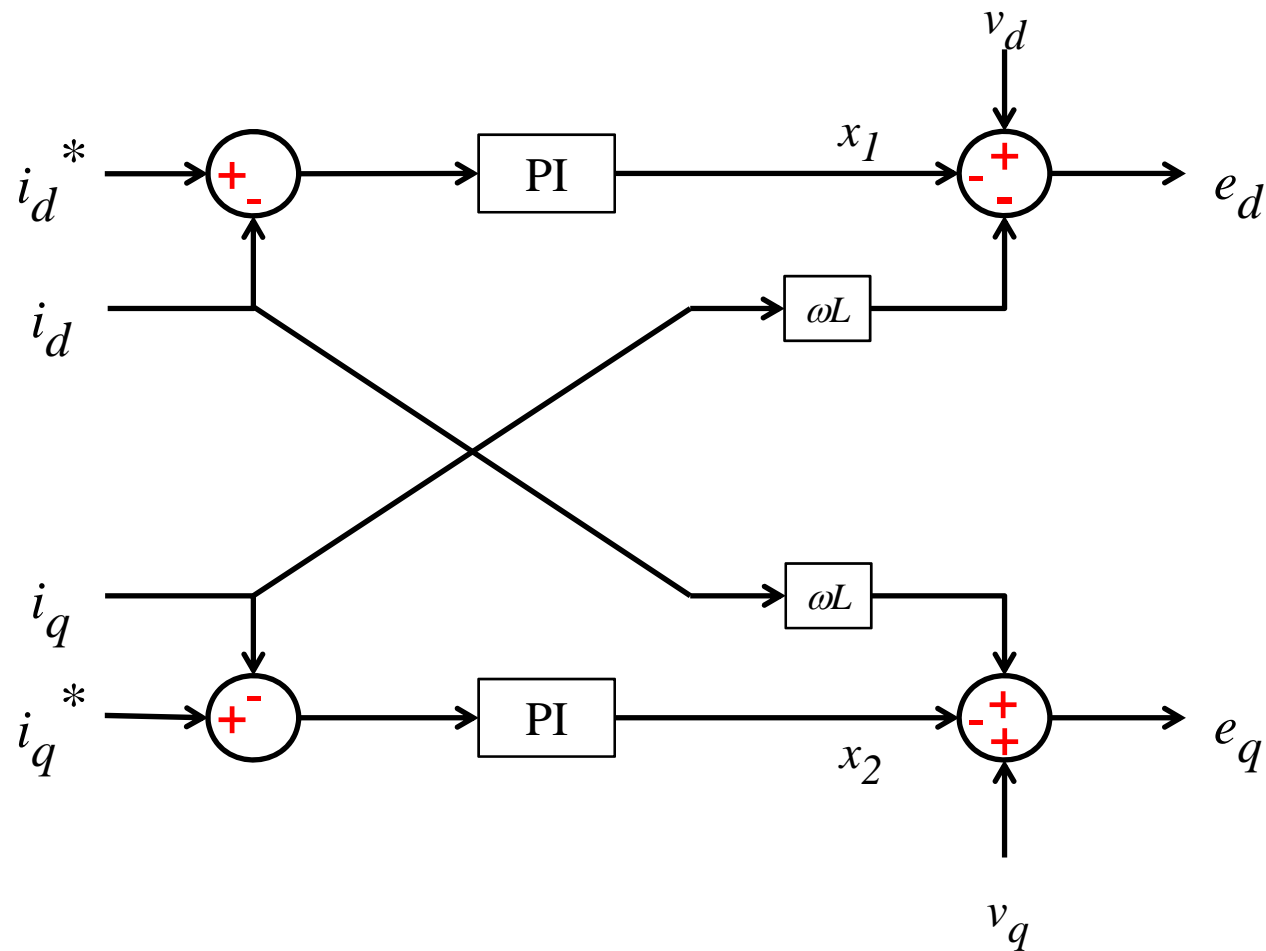
Current vector control with PLL locking to phase A voltage (cosine function)





Modular multilevel converters

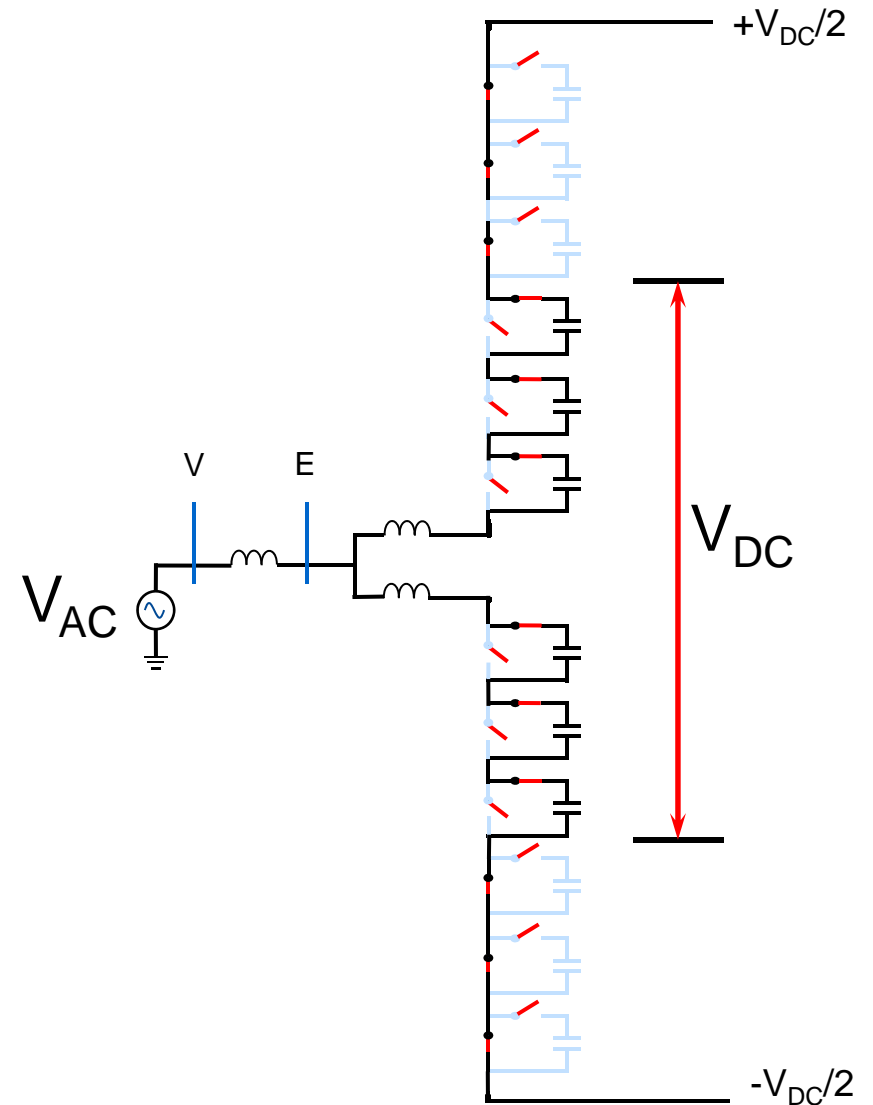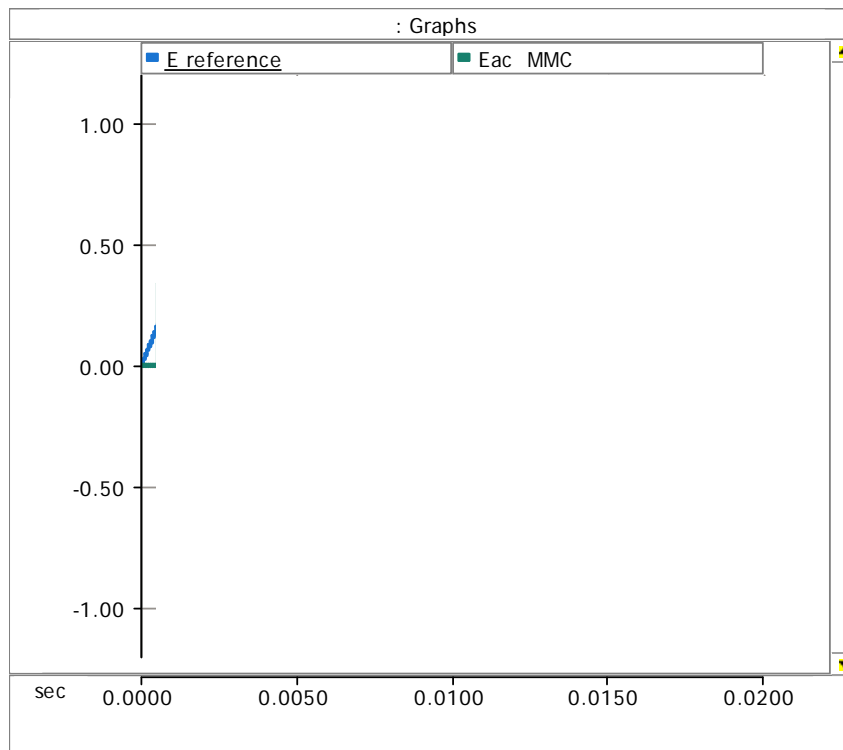



Modular multilevel converters

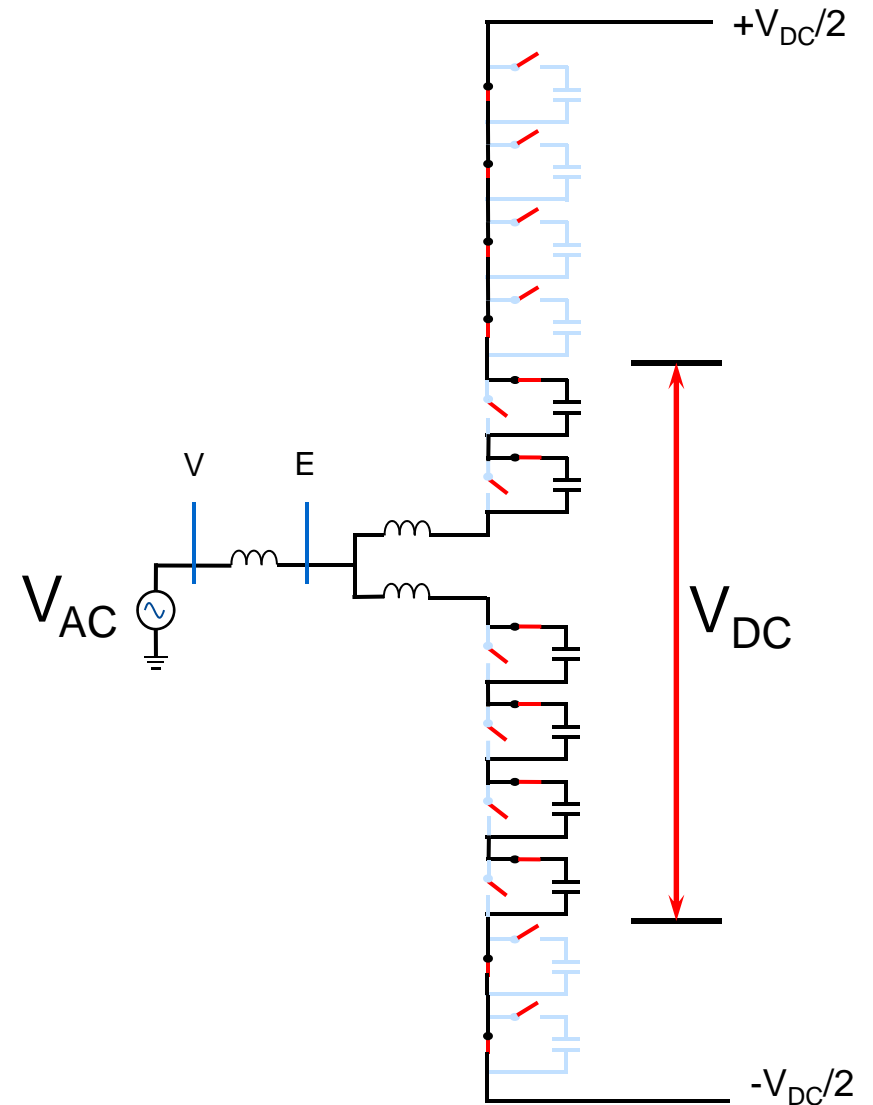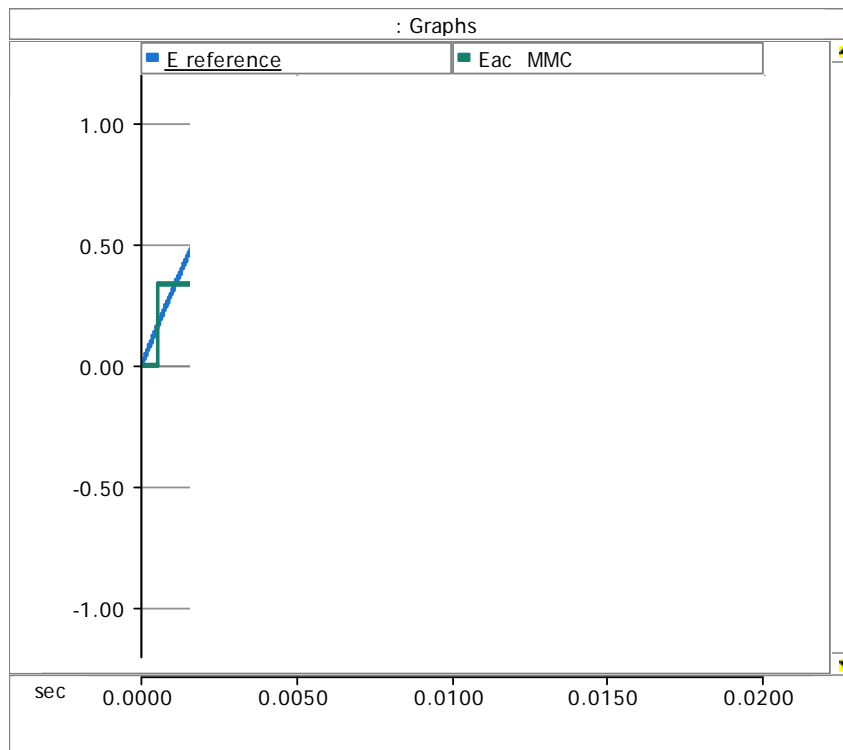



Modular multilevel converters

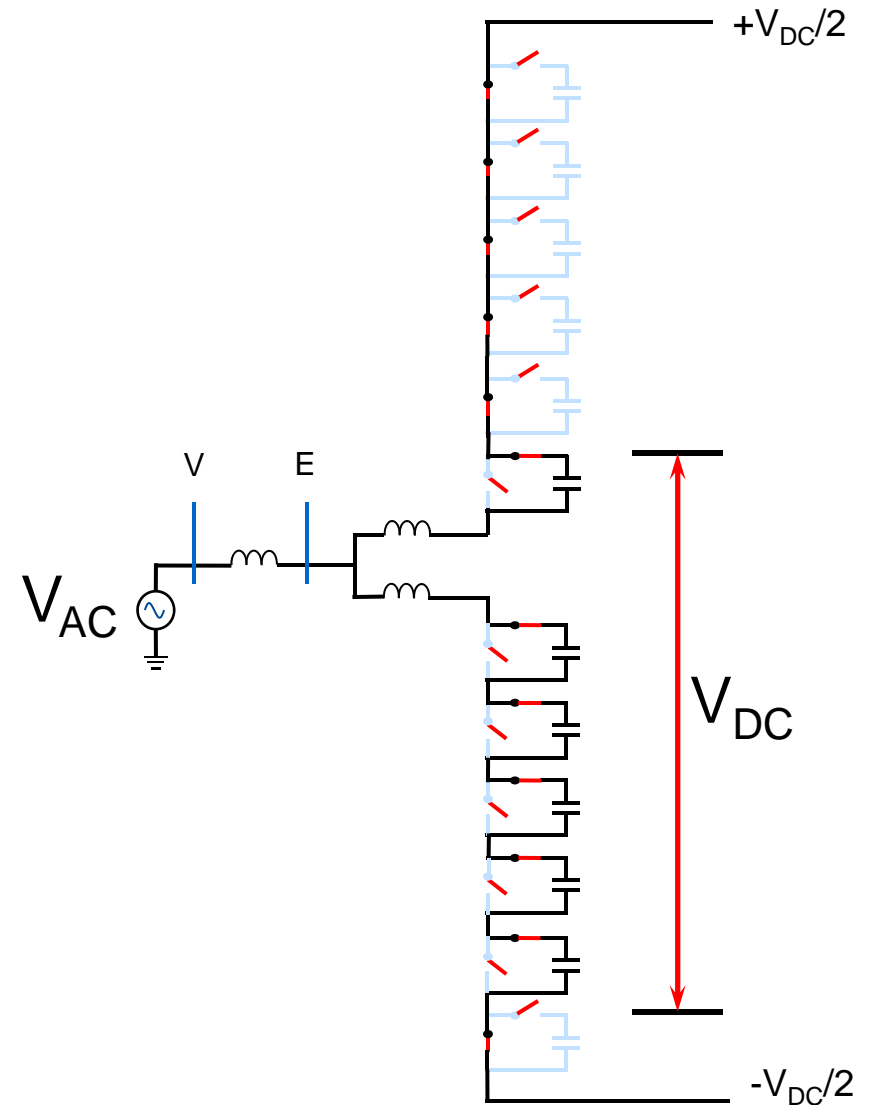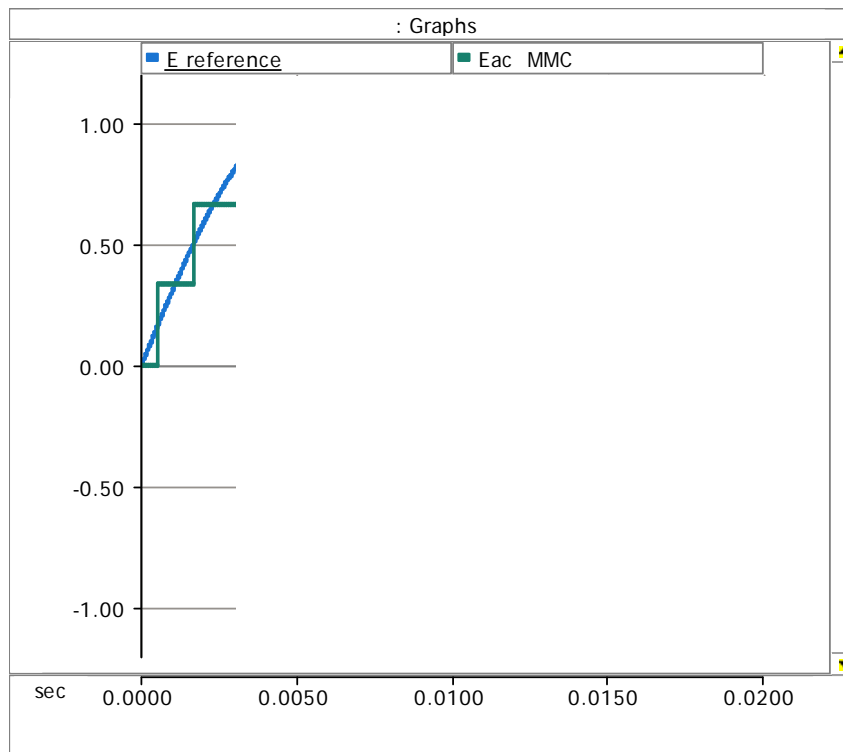



Modular multilevel converters

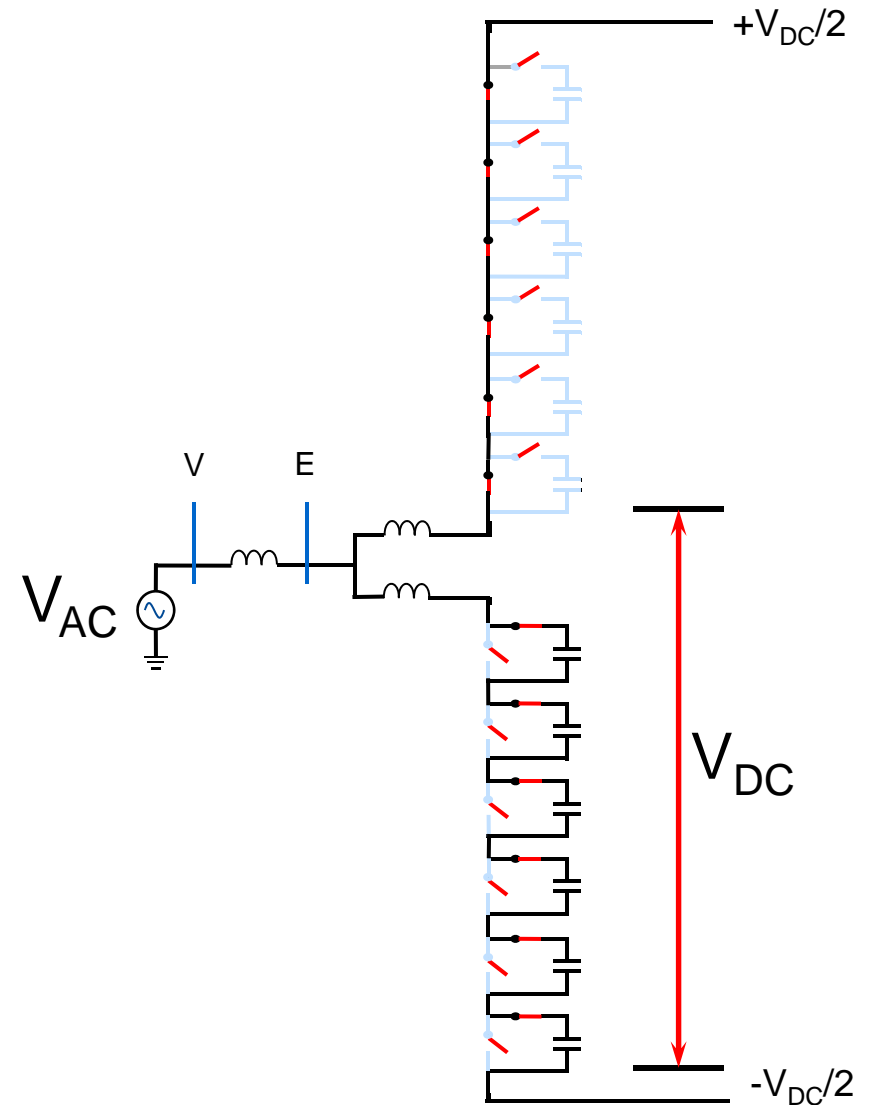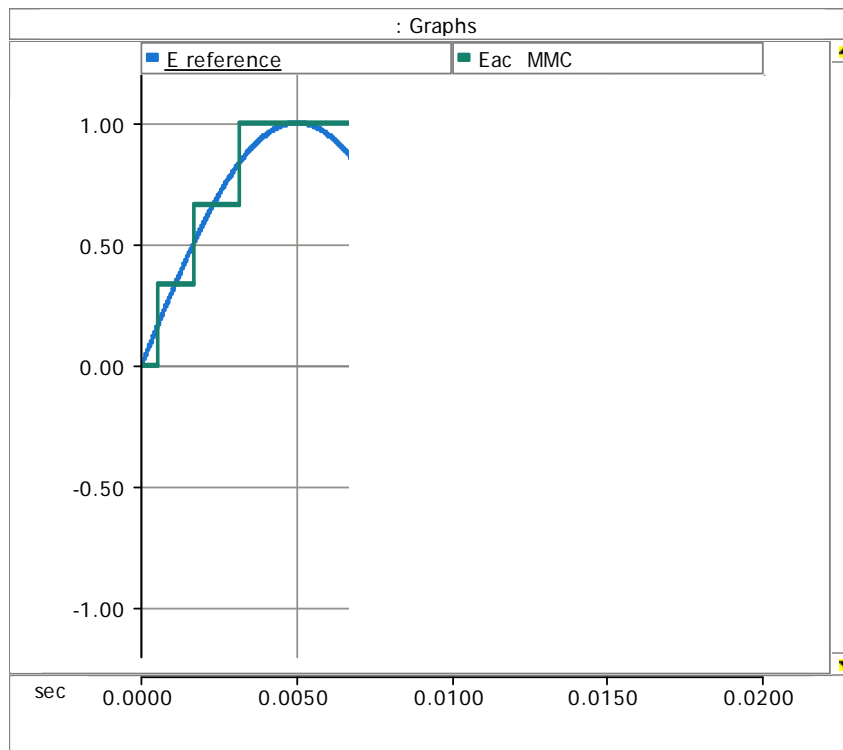



Modular multilevel converters

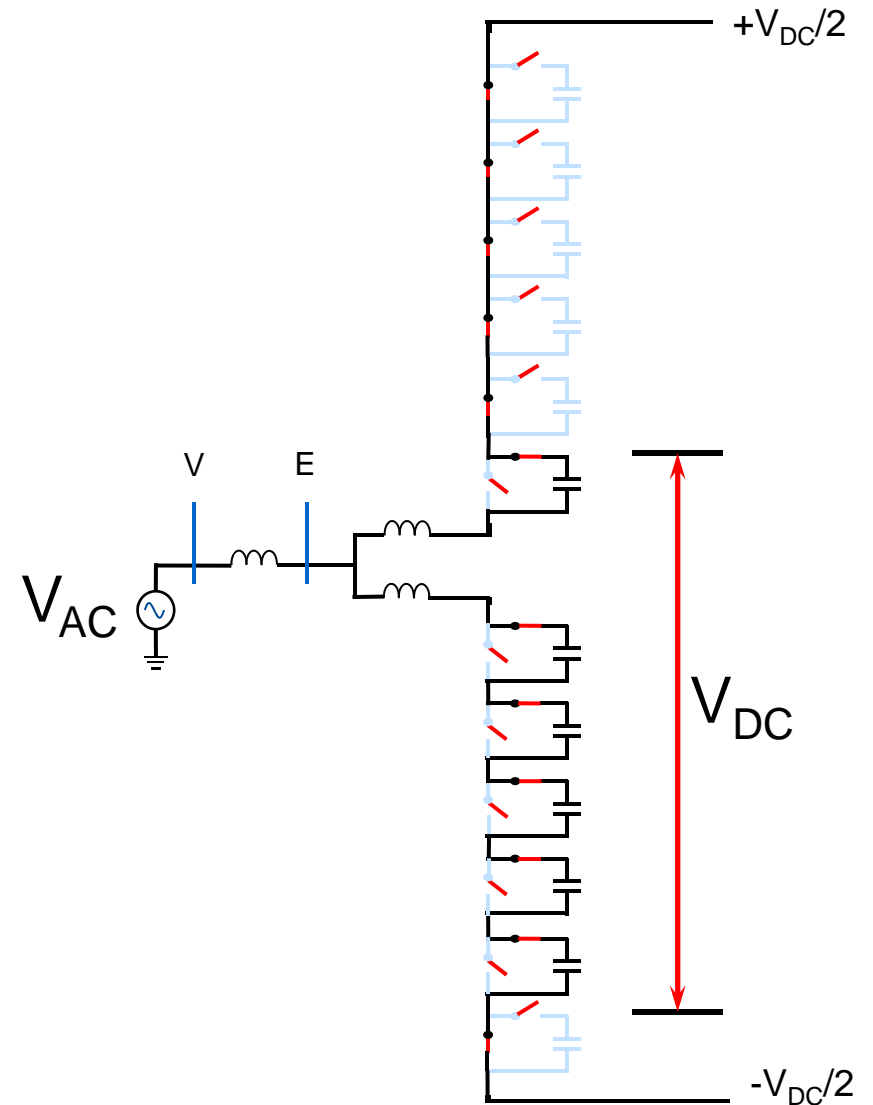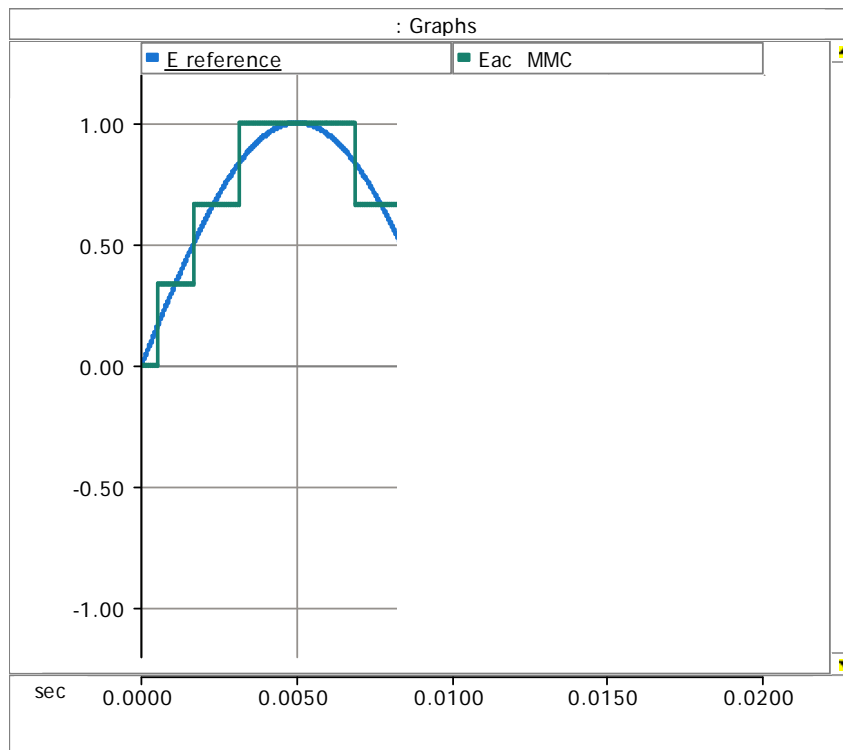



Modular multilevel converters

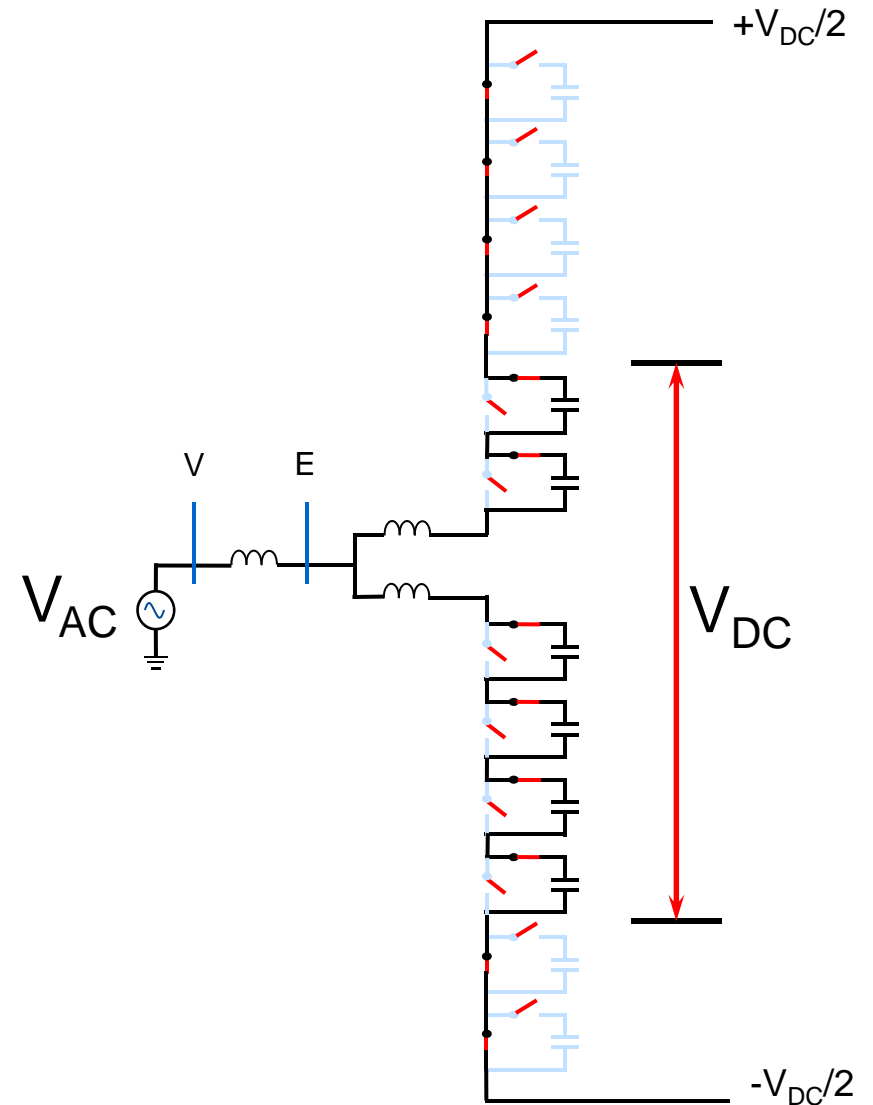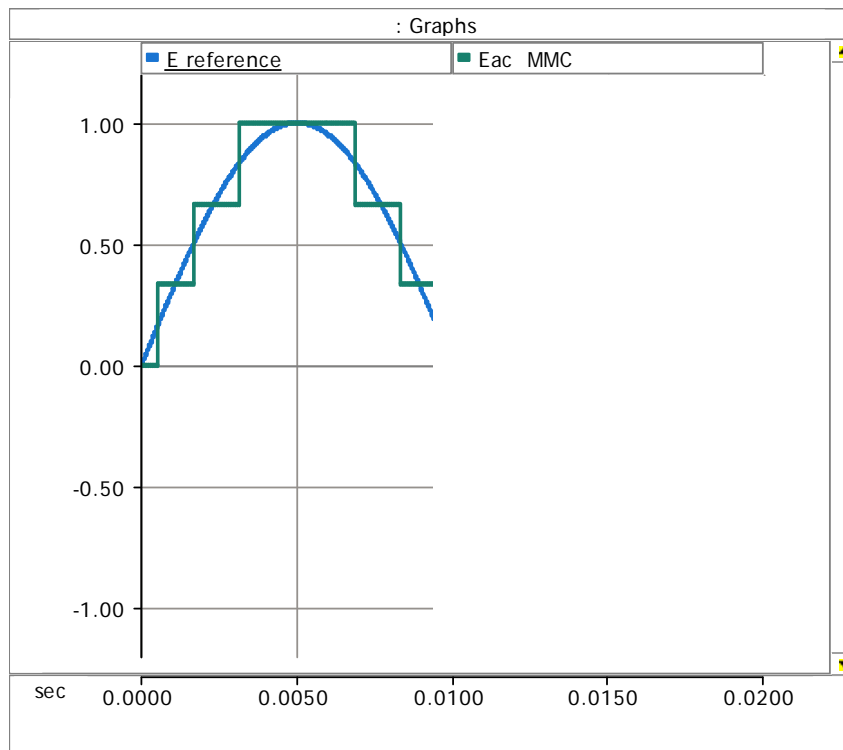



Modular multilevel converters

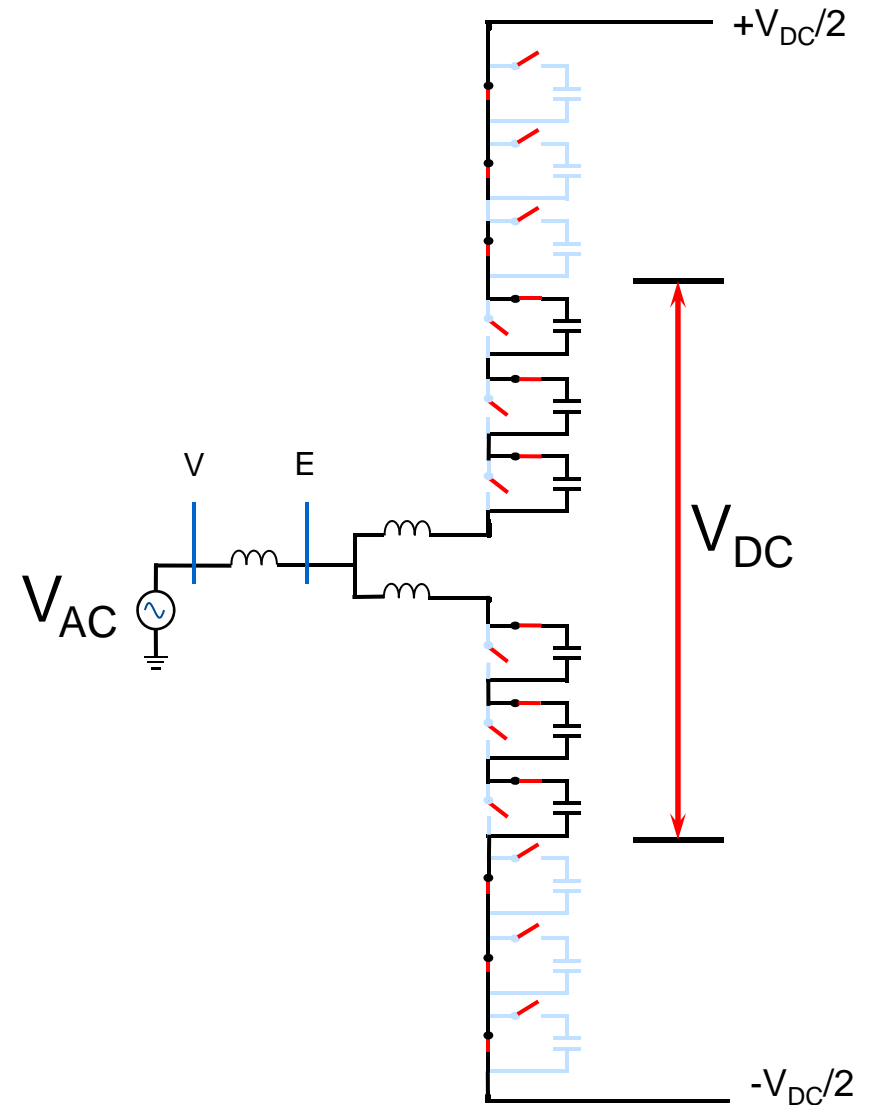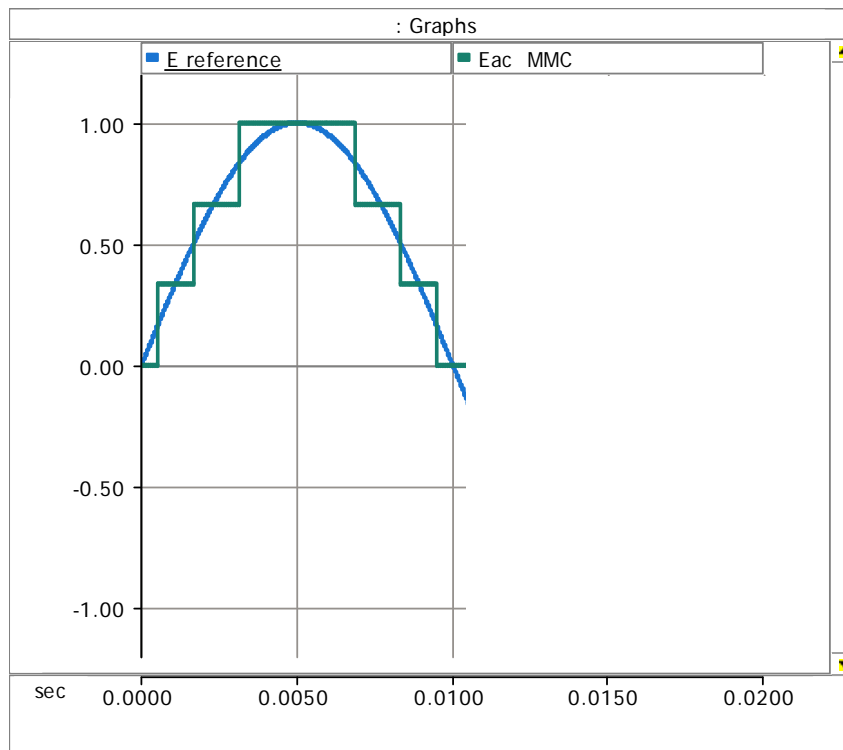



Modular multilevel converters

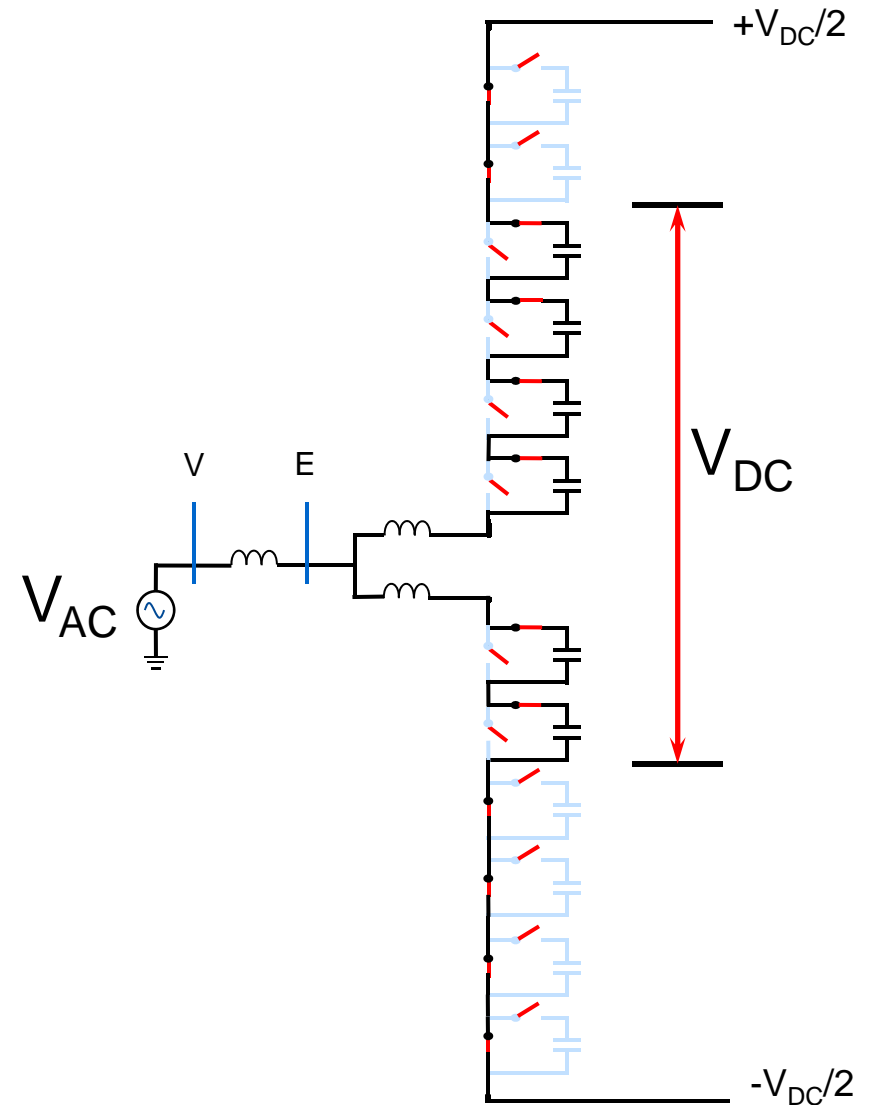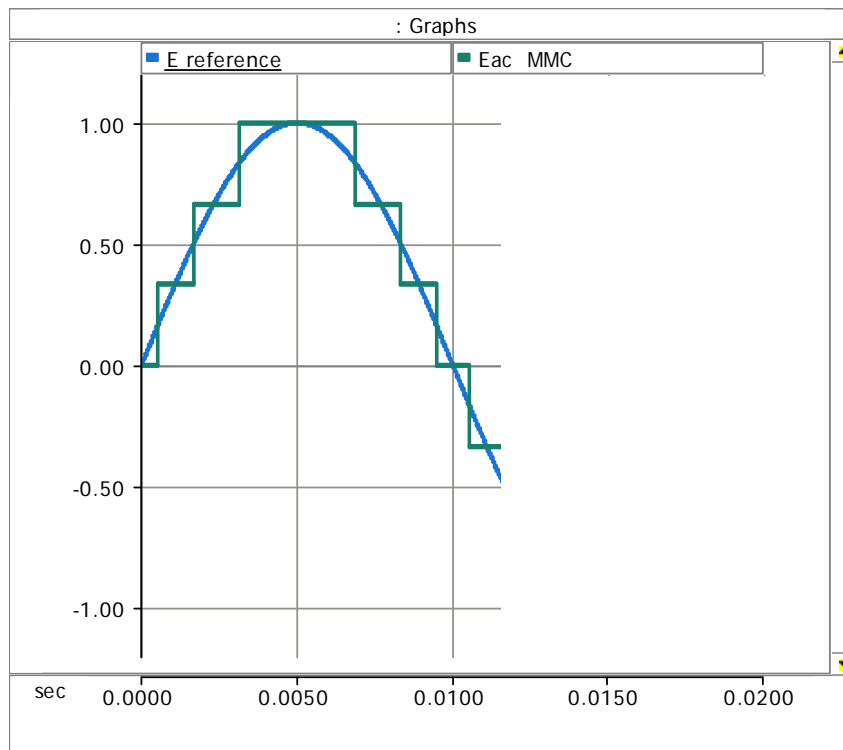



Modular multilevel converters

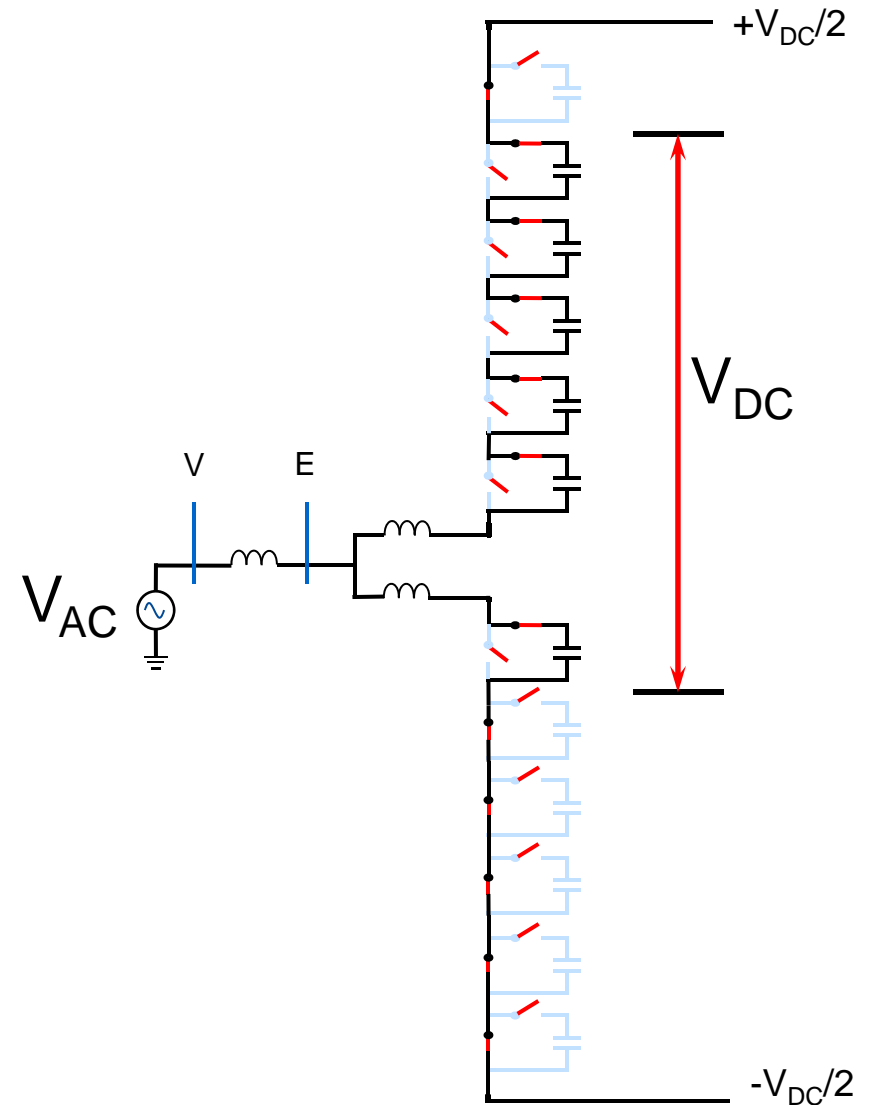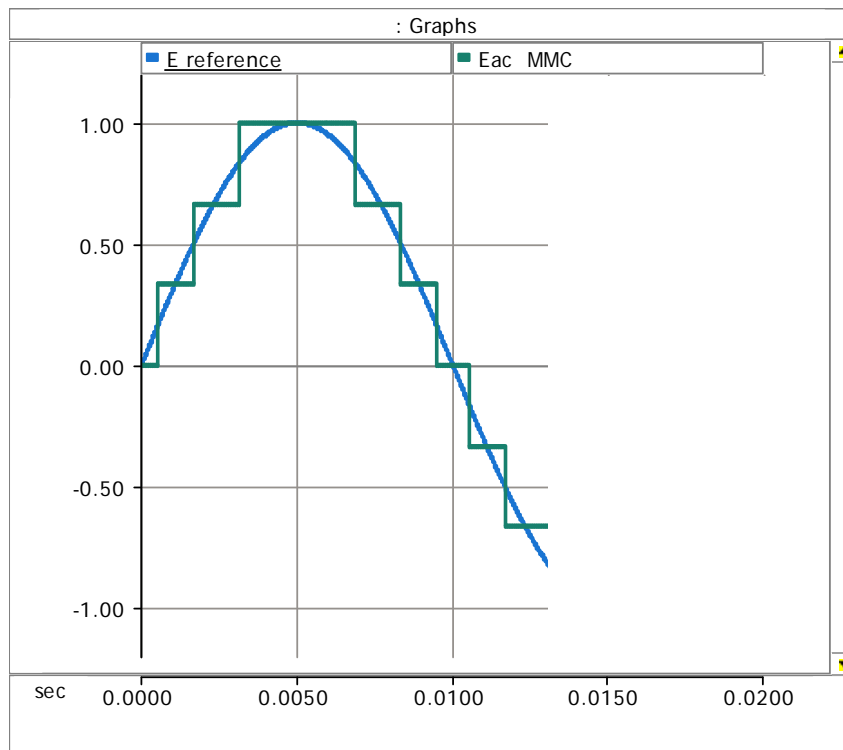



Modular multilevel converters

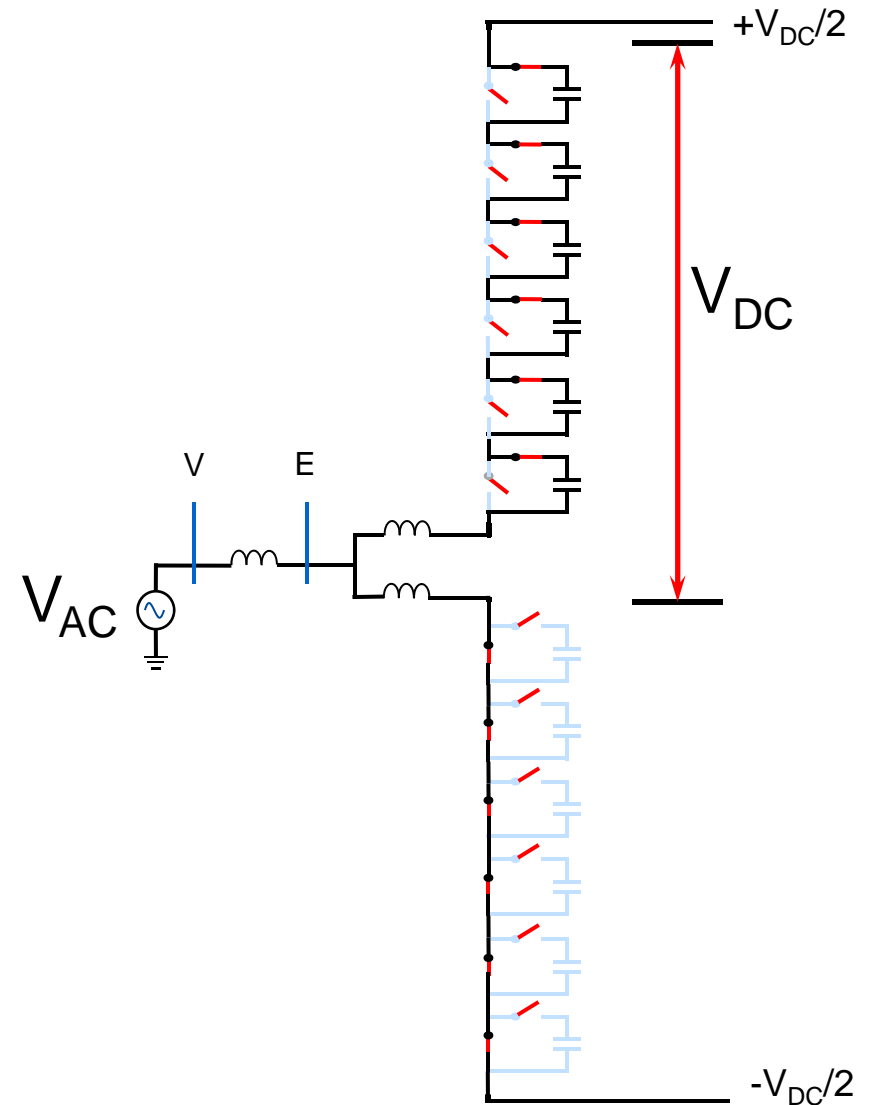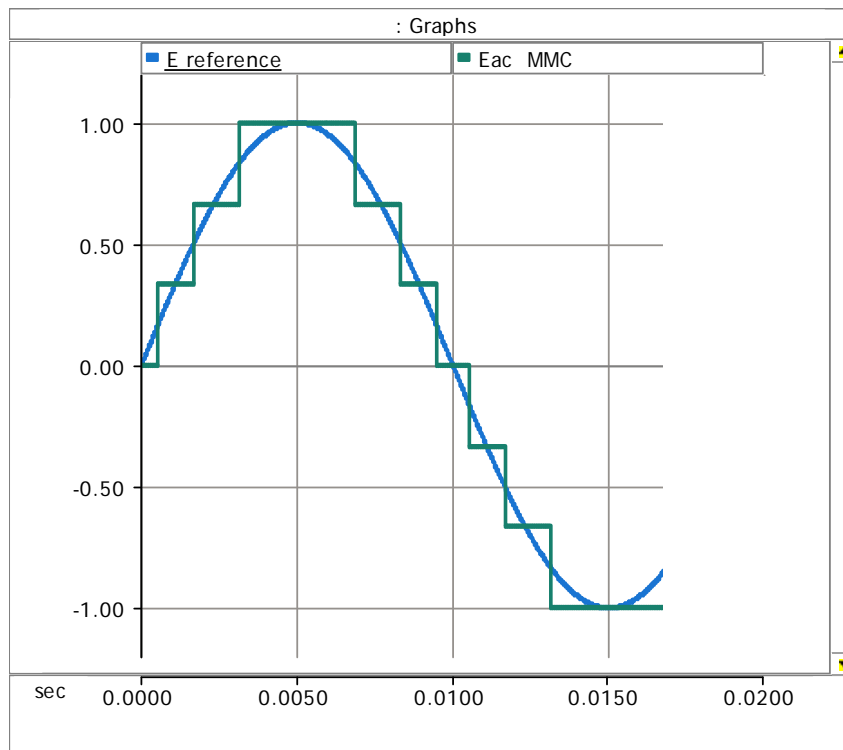



Modular multilevel converters

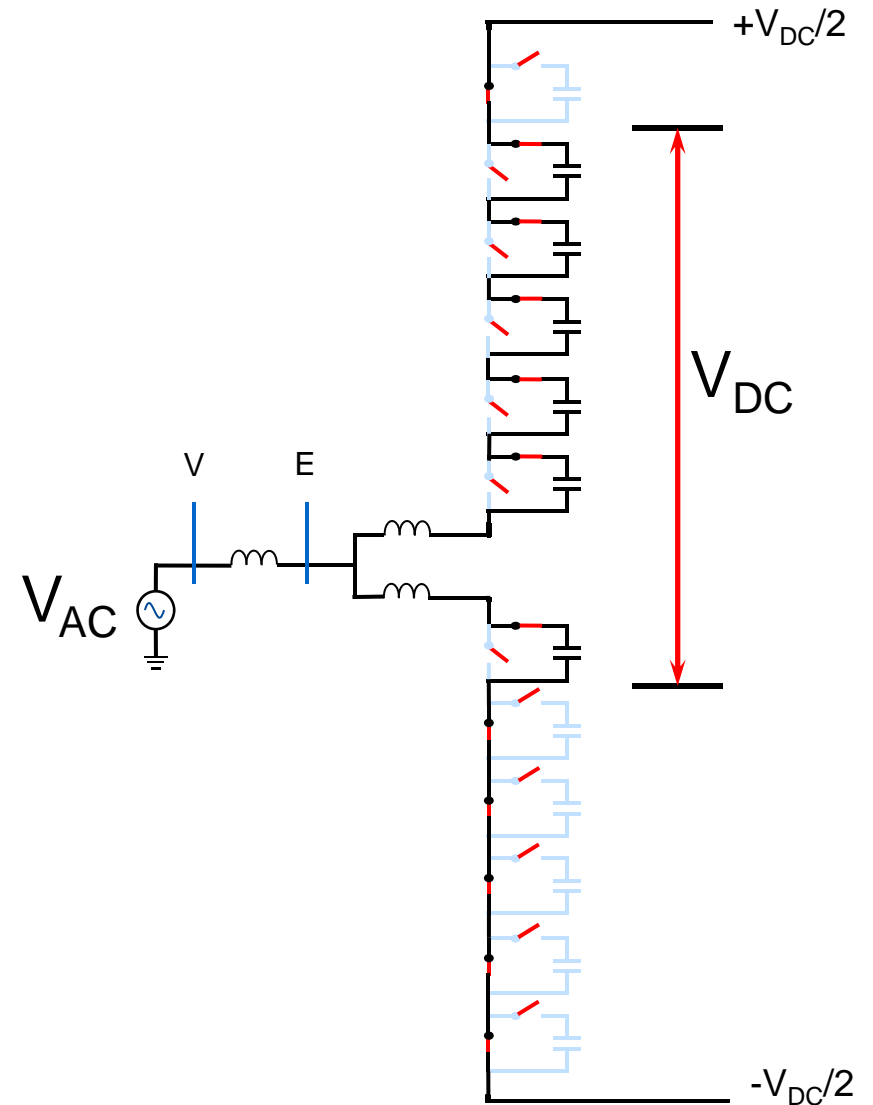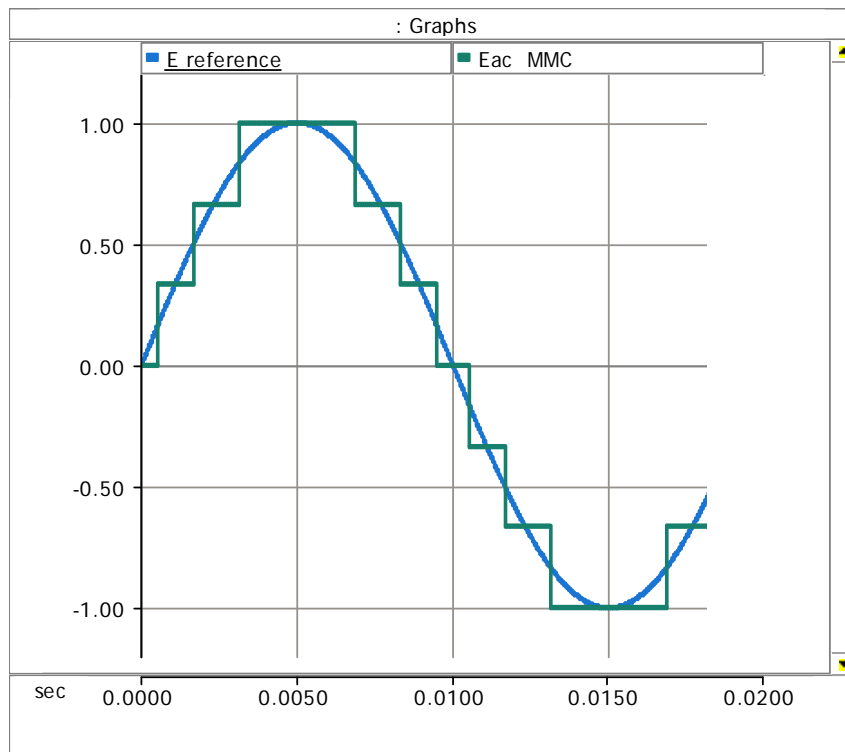

Modular multilevel converters

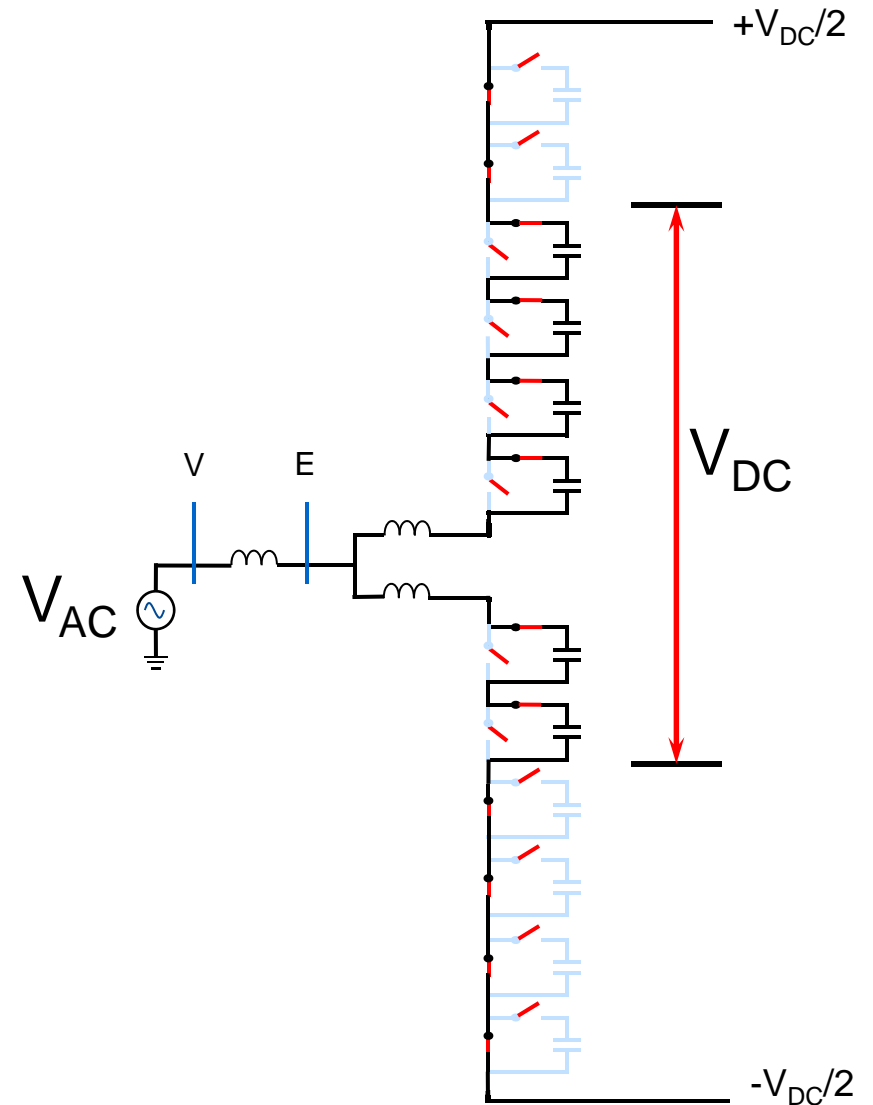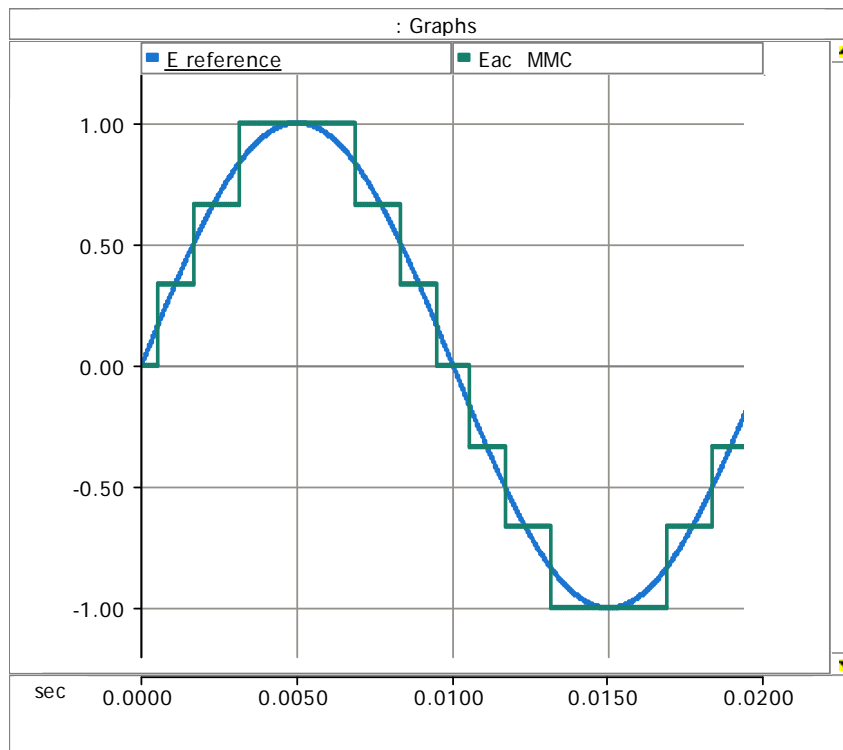


Modular multilevel converters

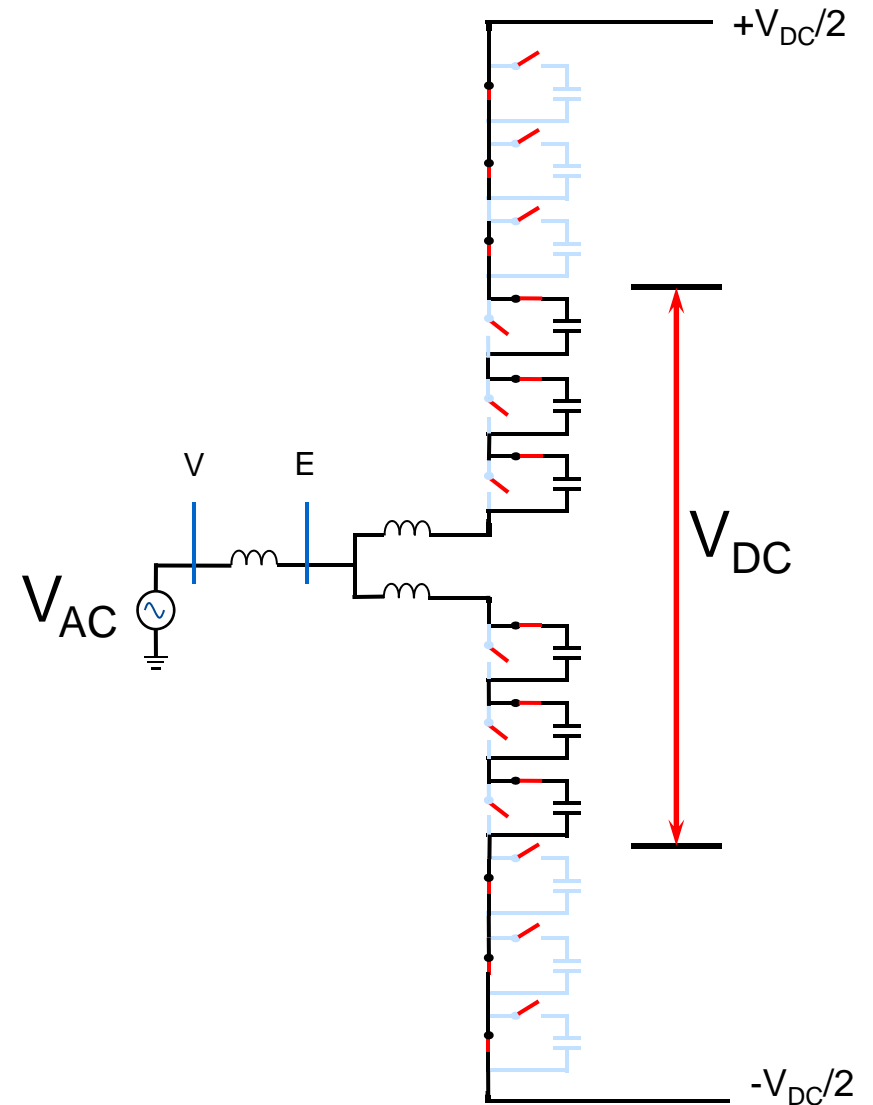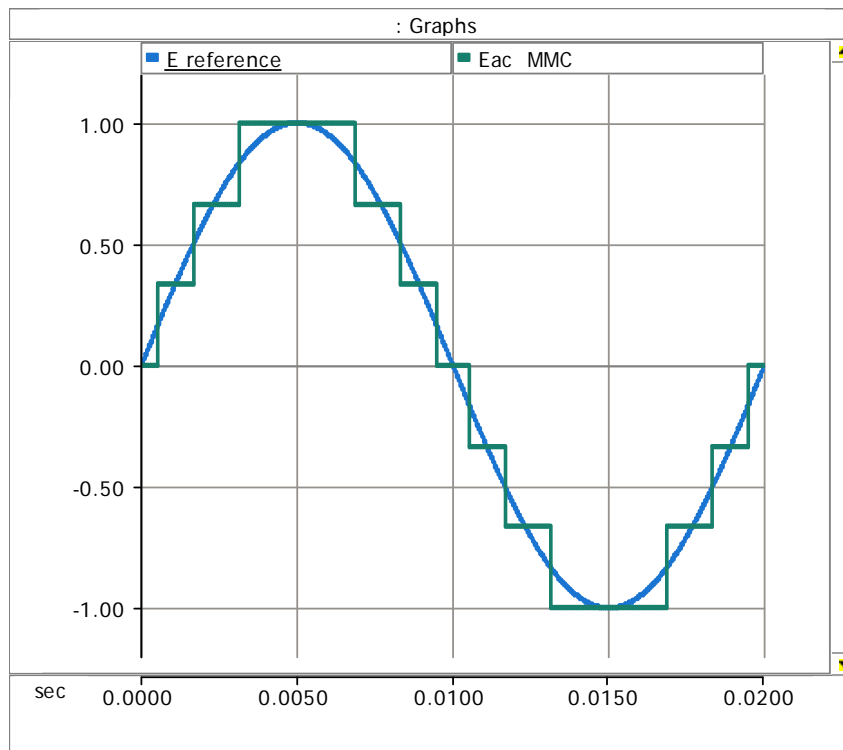

Types of MMC

Half-Bridge MMC 2009

Siemens diagram

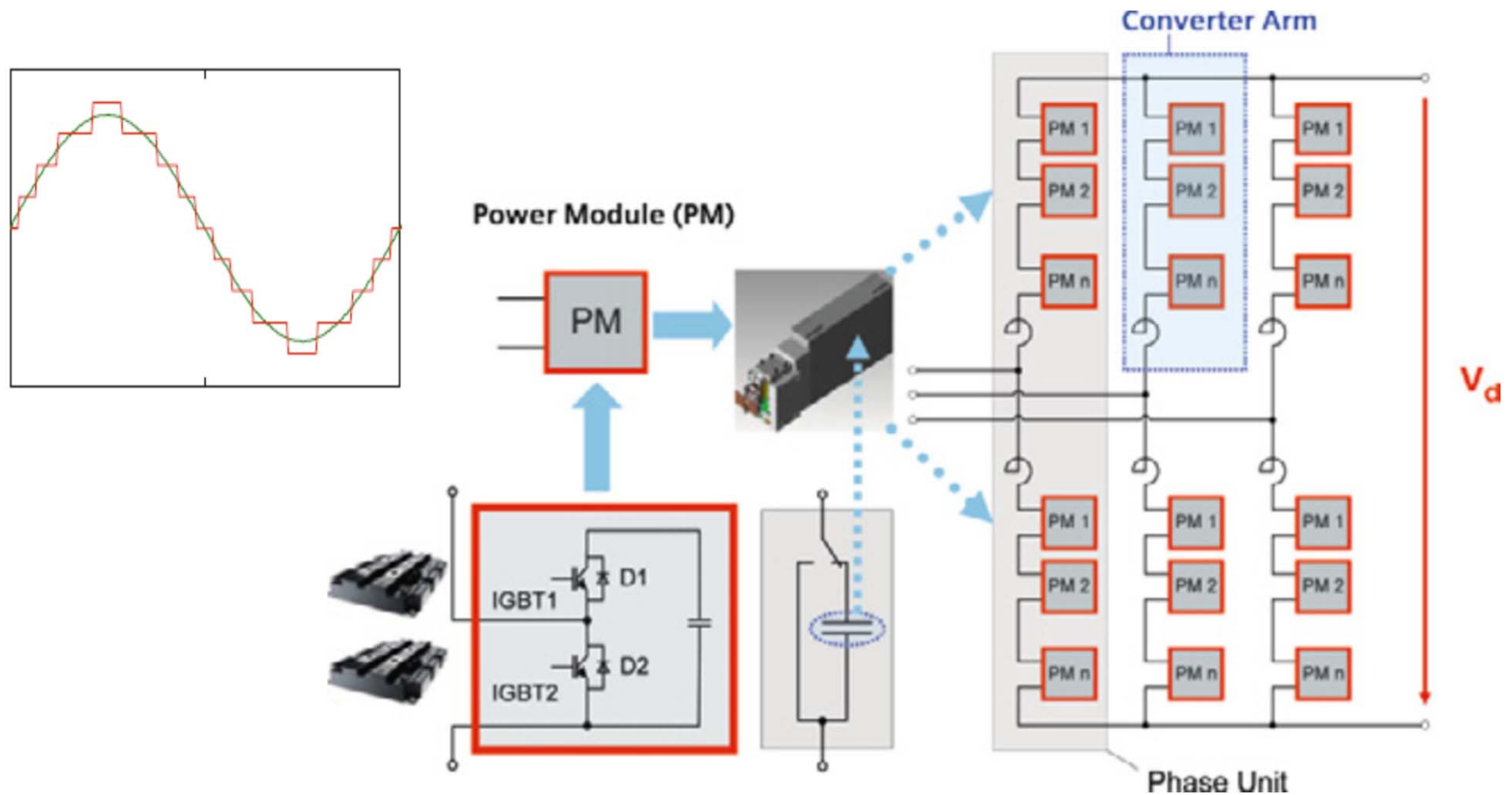


Note: Filters not required

VSC Valves: MMC



Full- or H-bridge cells

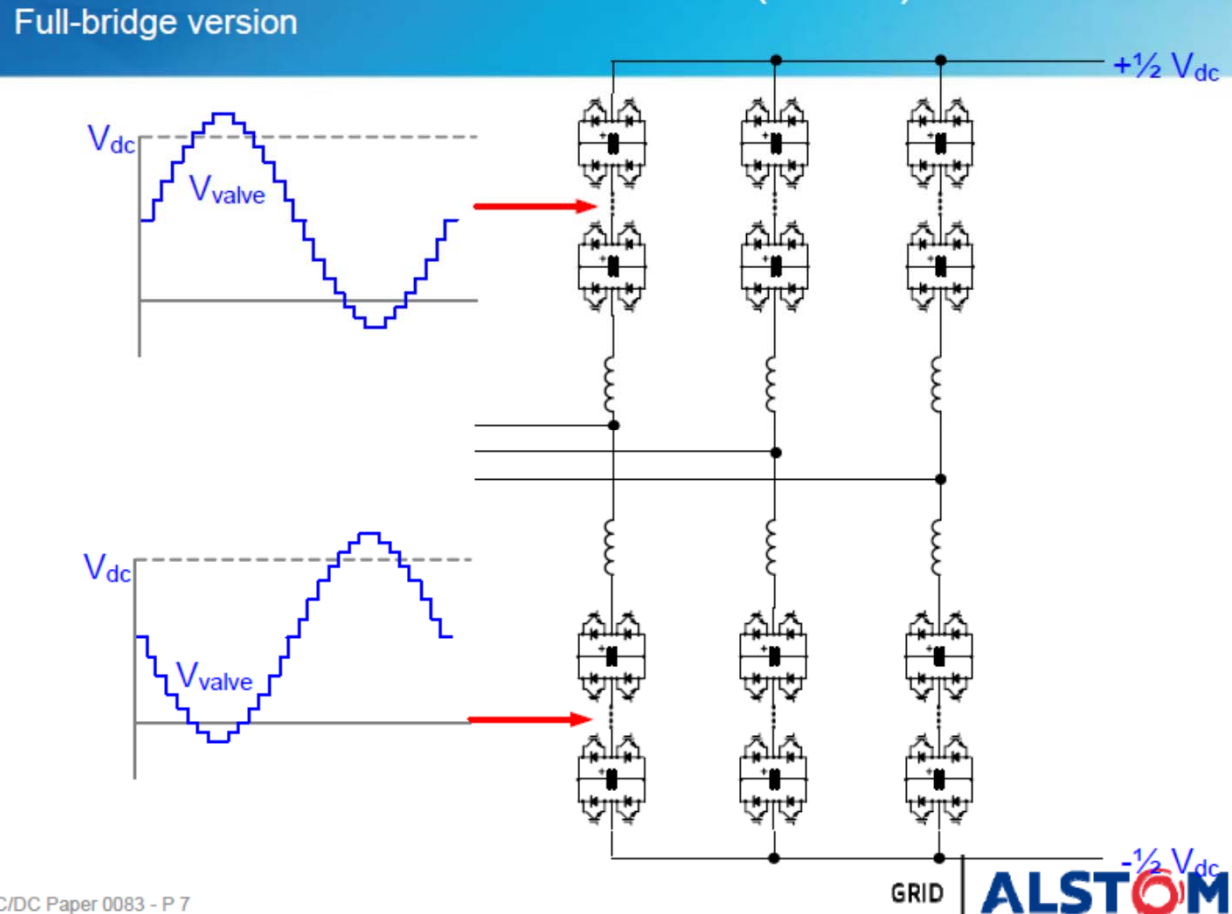Modular Multi-Level Converter (MMC) Full-bridge version



AC/DC Paper 0083 - P 7



Half-bridge MMC

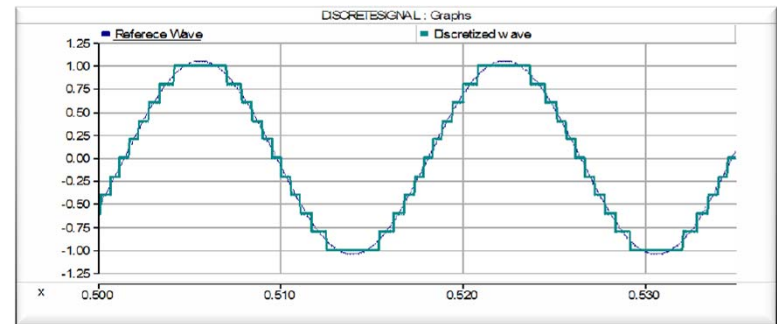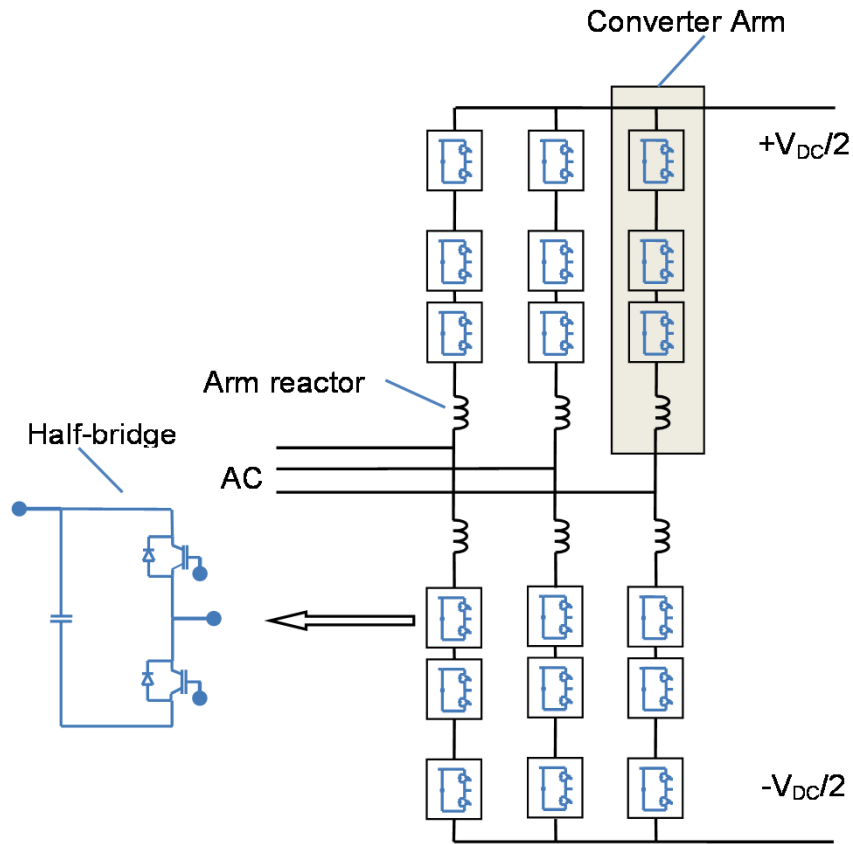


Half-bridge MMC

Three operating states in the half-bridge cell

State description	Gates
Insert +Vc	(T2)
Bypass capacitor	(T1)
Blocked	None
Forbidden	(T1,T2)

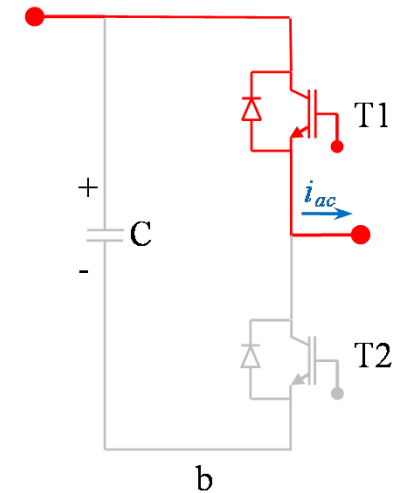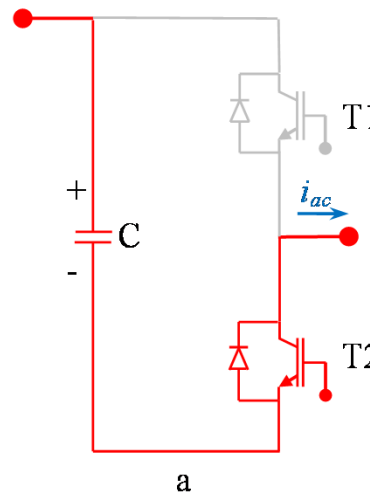


Half-bridge MMC

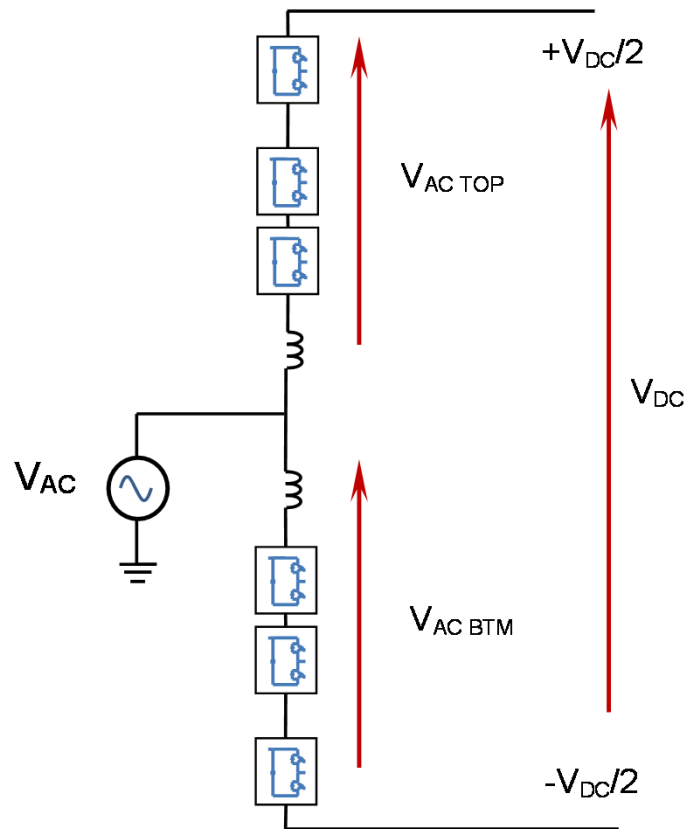

$$V_{AC\ TOP} = \frac{V_{DC}}{2} - V_{AC}$$

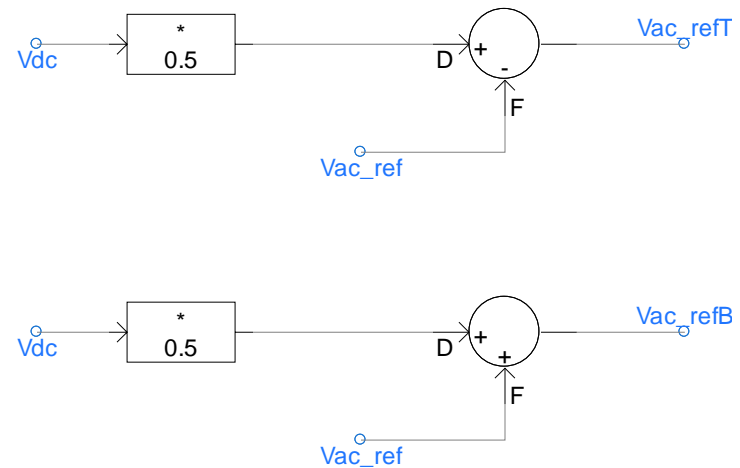
$$V_{AC\ BTM} = \frac{V_{DC}}{2} + V_{AC}$$



Note: Half-bridge **CAN NOT** generate $V_{DC} = 0$

Half-bridge MMC

Assuming modulating index = 1

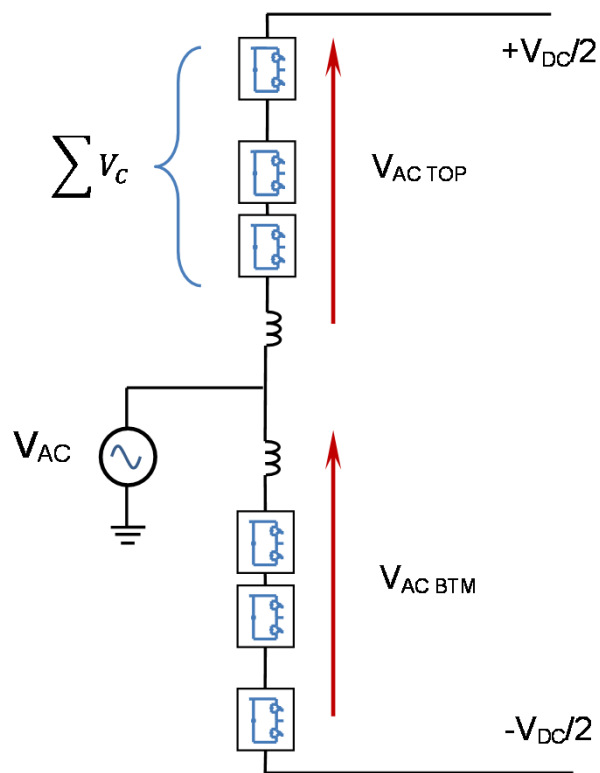

$$V_{AC \text{ PEAK}} = \frac{V_{DC}}{2}$$


$$V_{AC \text{ TOP}} = \frac{V_{DC}}{2} - V_{AC}$$

$$V_{AC \text{ BTM}} = \frac{V_{DC}}{2} + V_{AC}$$

V_{AC}	$V_{AC \text{ TOP}}$	$V_{AC \text{ BTM}}$
$+V_{DC}/2$	0	V_{DC}
0	$V_{DC}/2$	$V_{DC}/2$
$-V_{DC}/2$	V_{DC}	0


$$\sum V_C = V_{DC}$$

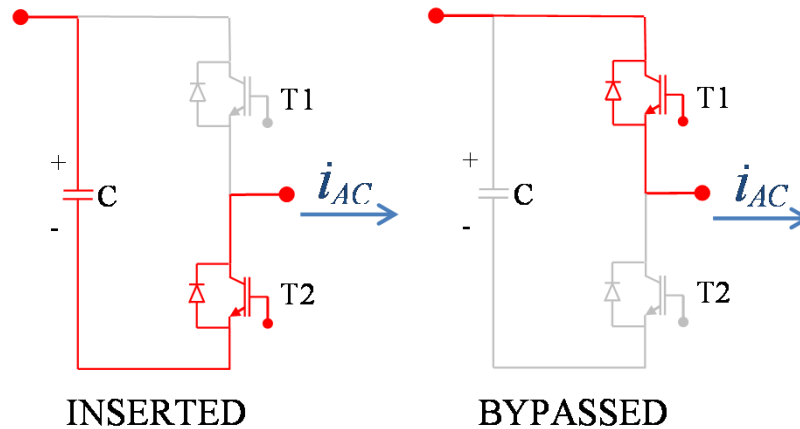Capacitor balancing: sorting method – Half-bridge cell



	$i_{ac} < 0$	$i_{ac} > 0$
Inserted cell	Discharges capacitor	Charges capacitor
Bypassed cell	Prevents discharging of capacitor	Prevents charging of capacitor

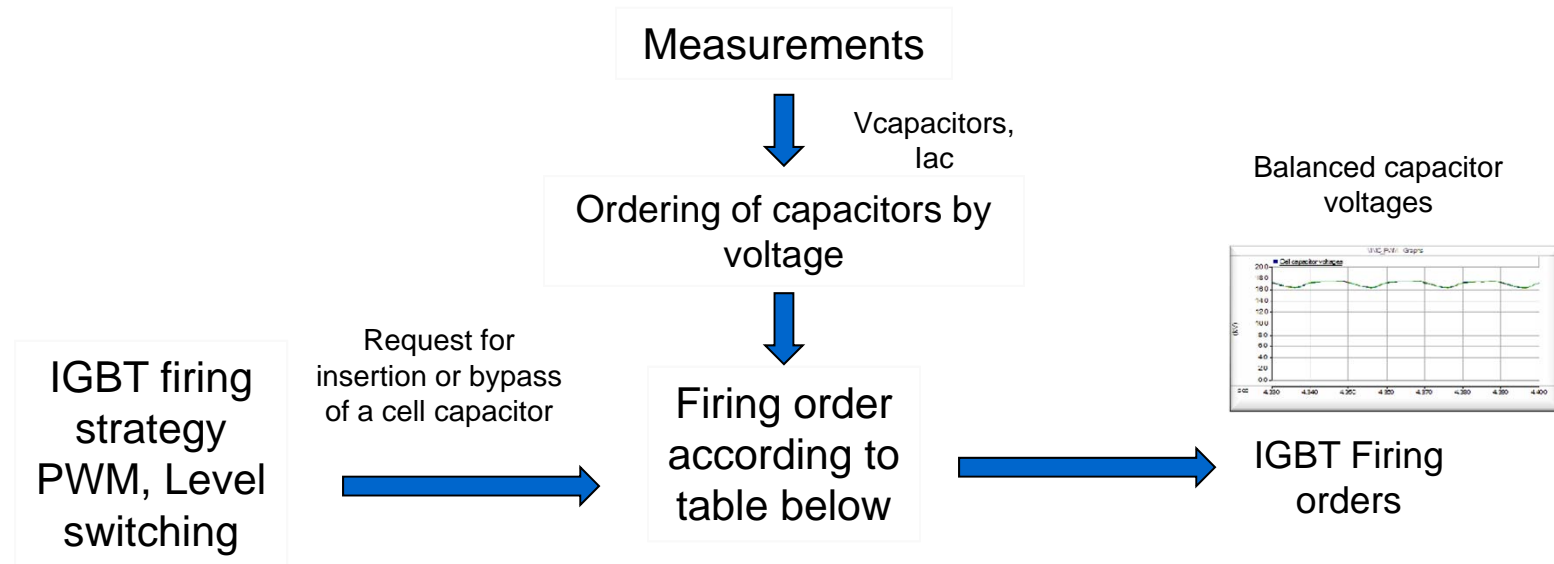
Capacitor balancing: sorting method – Half-bridge cell



Action requested	$i_{ac} < 0$	$i_{ac} > 0$
Insert cell	Insert cell with highest voltage	Insert cell with lowest voltage
Bypass cell	Bypass cell with lowest voltage	Bypass cell with highest voltage


Low Level Controls

Stages

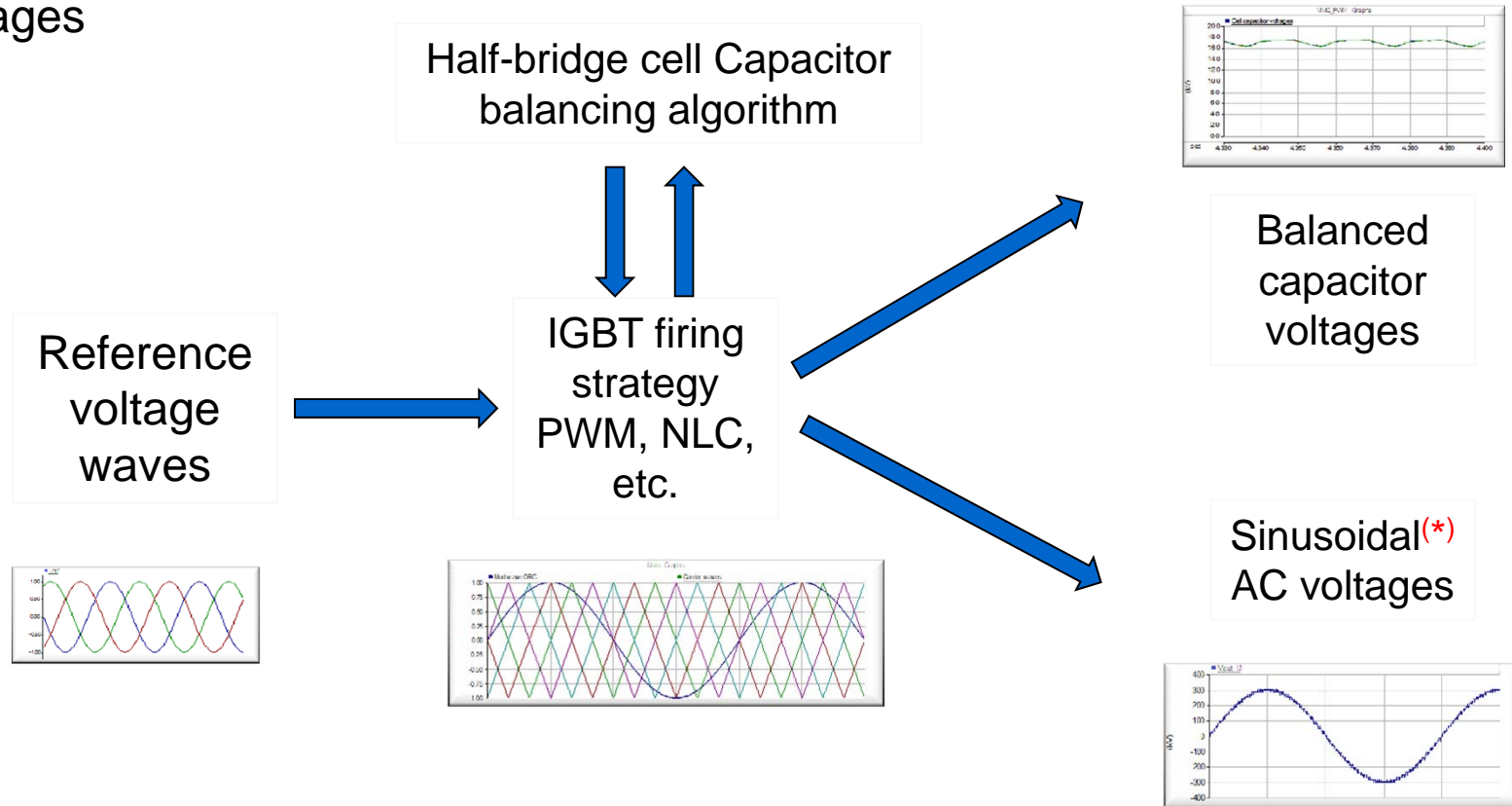

(*) or with harmonic content
as required


H-bridge MMC (full-bridge)

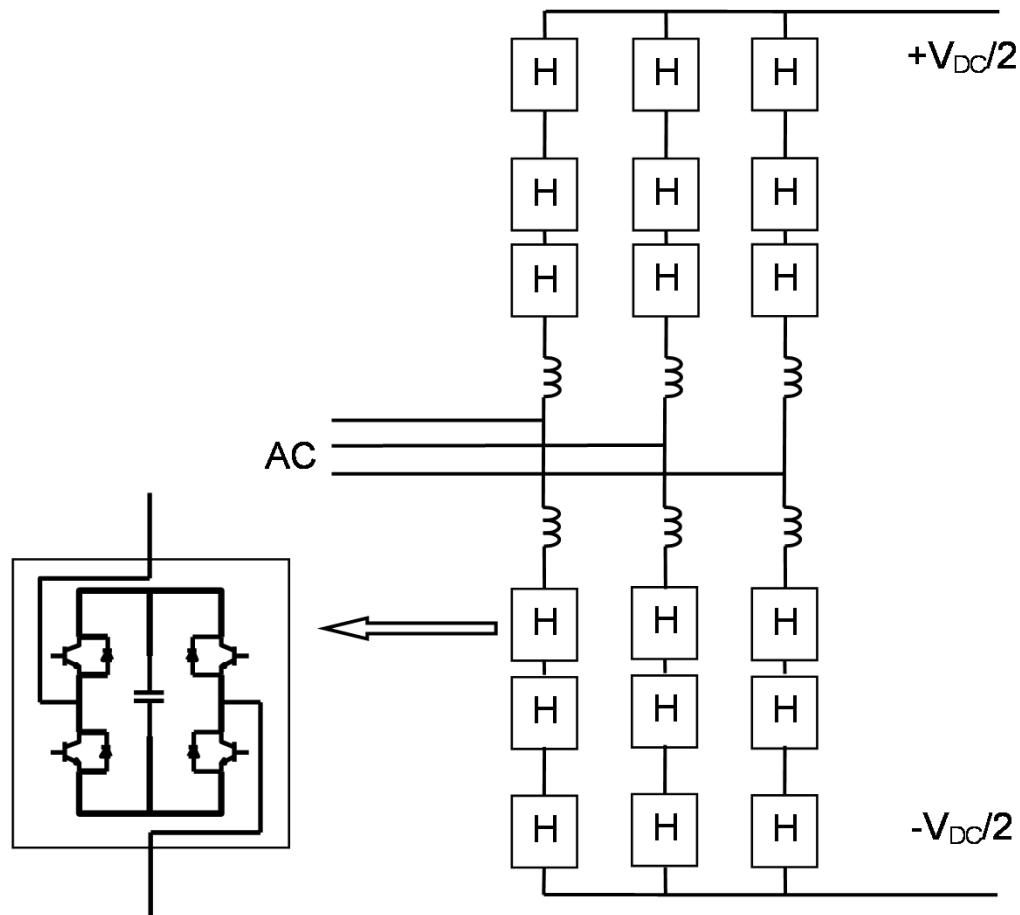


H-bridge

Four operating states

State description	Gates
Insert +Vc	(T1,T4)
Insert -Vc	(T3,T2)
Bypass capacitor	(T1,T2) or (T3,T4)
Blocked	None
Forbidden	(T1,T3) & (T2,T4)

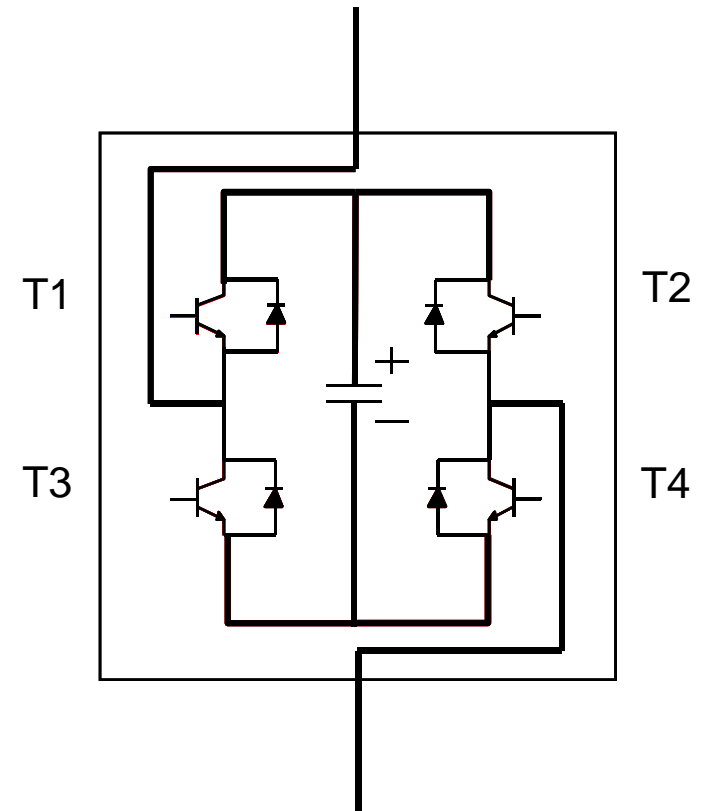


H-bridge

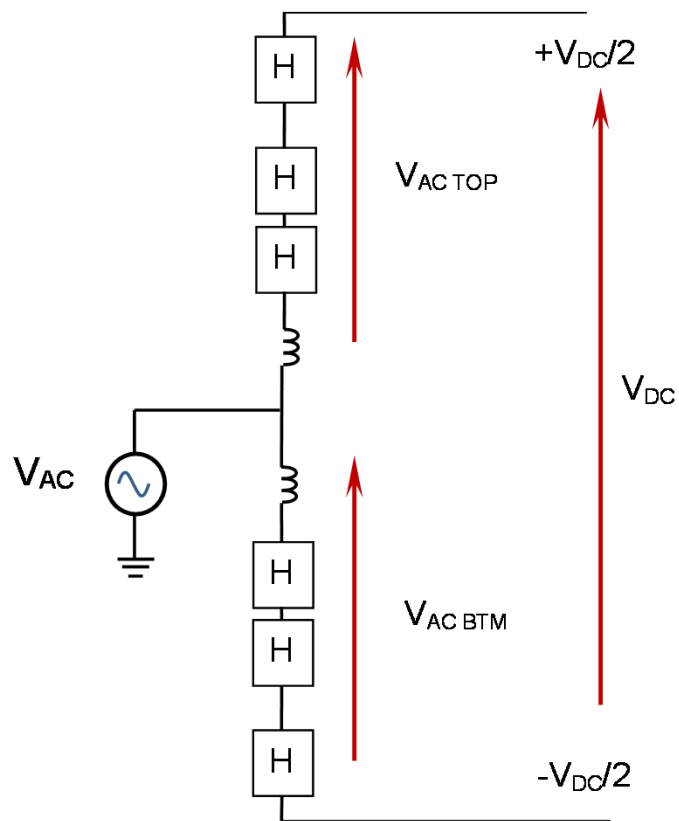


$$V_{AC \text{ TOP}} = \frac{V_{DC}}{2} - V_{AC}$$
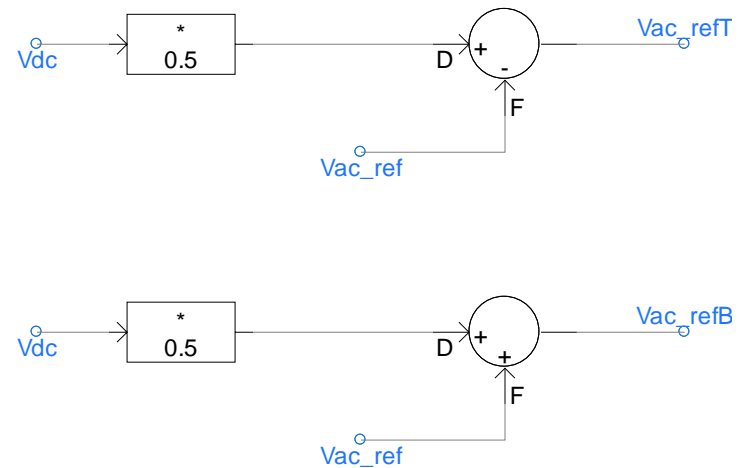
$$V_{AC \text{ BTM}} = \frac{V_{DC}}{2} + V_{AC}$$



Note: H-bridge **CAN** generate $V_{DC} = 0$

Half-bridge MMC

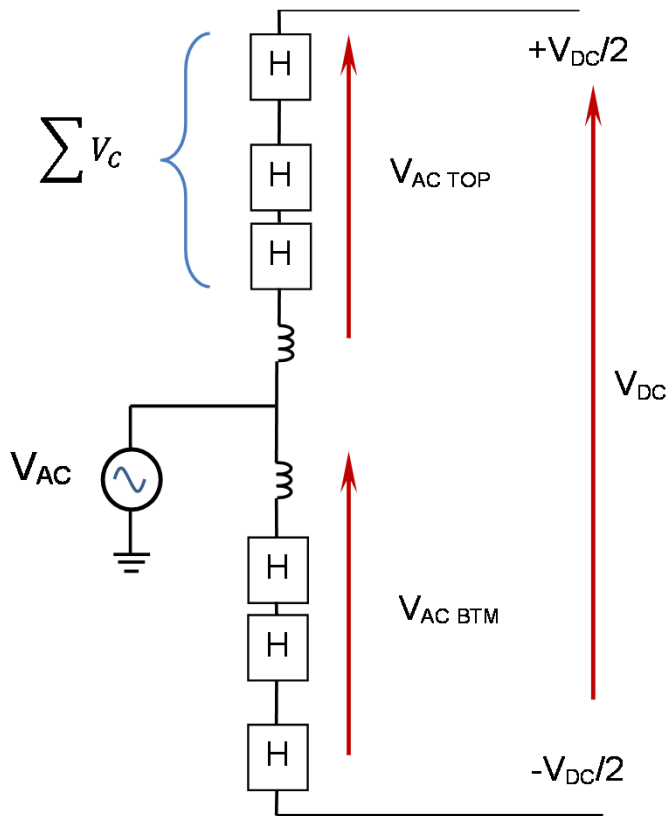

Assuming modulating index = 1.25

$$V_{AC \text{ PEAK}} = 1.25 \frac{V_{DC}}{2}$$



$$V_{AC \text{ TOP}} = \frac{V_{DC}}{2} - V_{AC} \quad V_{AC \text{ BTM}} = \frac{V_{DC}}{2} + V_{AC}$$

V_{AC}	$V_{AC \text{ TOP}}$	$V_{AC \text{ BTM}}$
$+1.25V_{DC}/2$	$-0.125V_{DC}$	$1.125V_{DC}$
$+V_{DC}/2$	0	V_{DC}
0	$V_{DC}/2$	$V_{DC}/2$
$-V_{DC}/2$	V_{DC}	0
$-1.25V_{DC}/2$	$1.125V_{DC}$	$-0.125V_{DC}$

$$\sum V_C = 1.125 \times V_{DC}$$

Modelling techniques: MMC valves

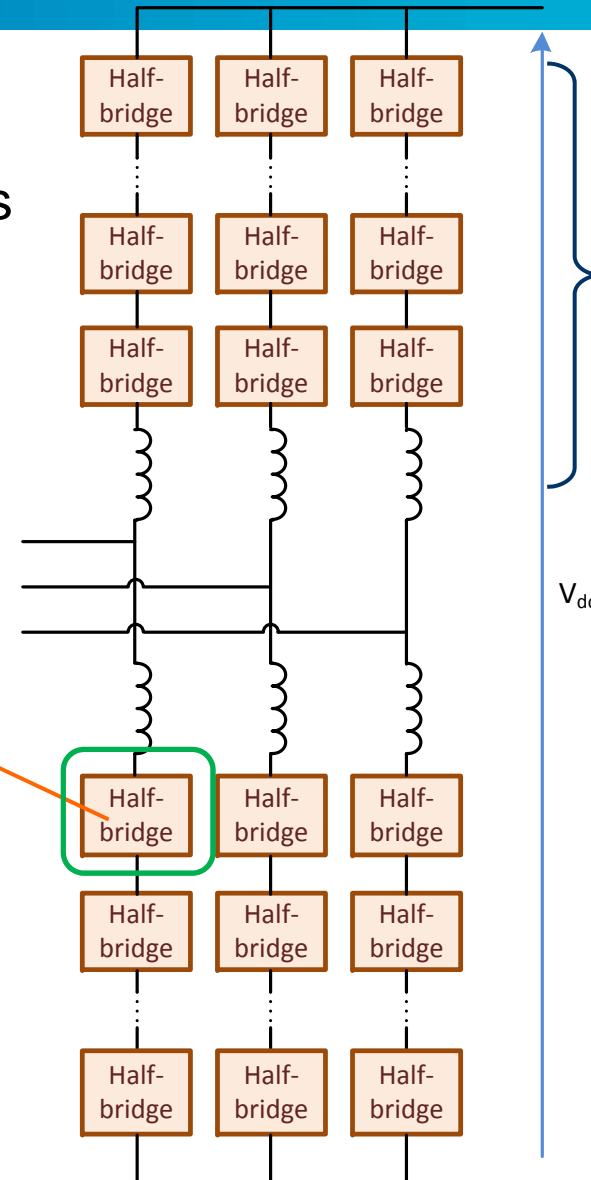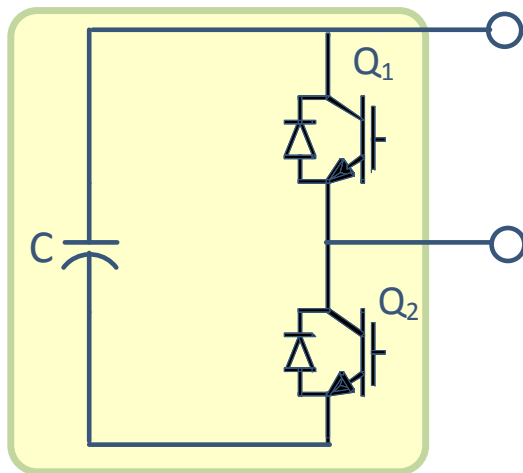- Simulation of MMC VSCs can involve hundreds of nodes. This significantly reduces simulation speed.




Can be in the order of a few hundred cells per arm

Modelling techniques: MMC valves

- Using Thevenin equivalent:
(detailed equivalent model)

$$R_{eq} = R_1 \left[1 - \frac{R_1}{R_1 + R_2 + R_C} \right]$$
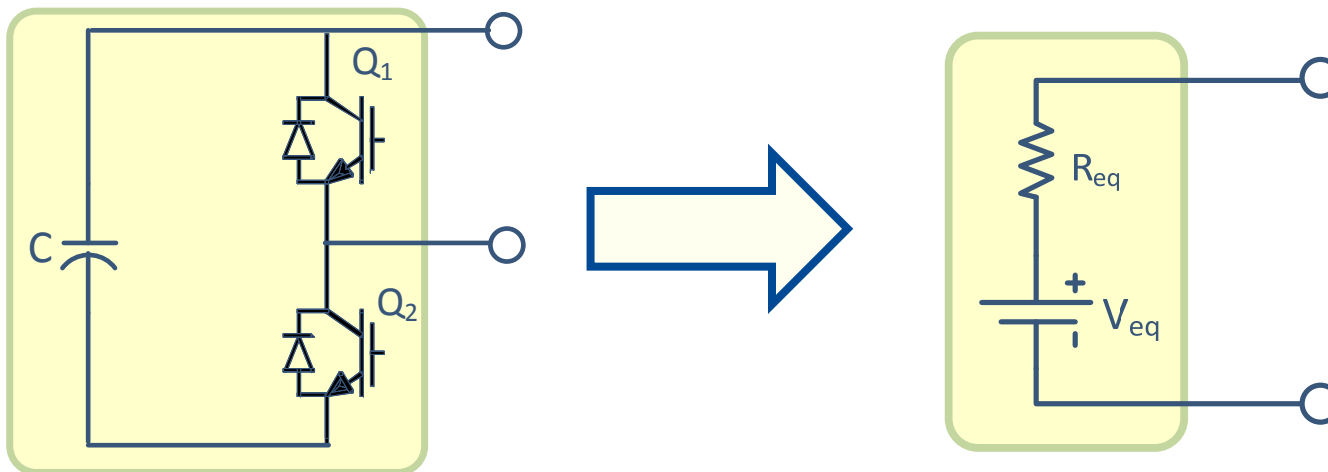
$$V_{eq} = \frac{R_1}{R_1 + R_2 + R_C} V_C$$




U. N. Gnanarathna, A. M. Gole, and R. P. Jayasinghe, "Efficient Modeling of Modular Multilevel HVDC Converters (MMC) on Electromagnetic Transient Simulation Programs," IEEE Transactions on Power Delivery, vol.26, no.1, pp.316-324, Jan. 2011

Modelling techniques: MMC valves

- Using Thevenin equivalent:
(detailed equivalent model)

$$R_{eq} = R_1 \left[1 - \frac{R_1}{R_1 + R_2 + R_C} \right]$$
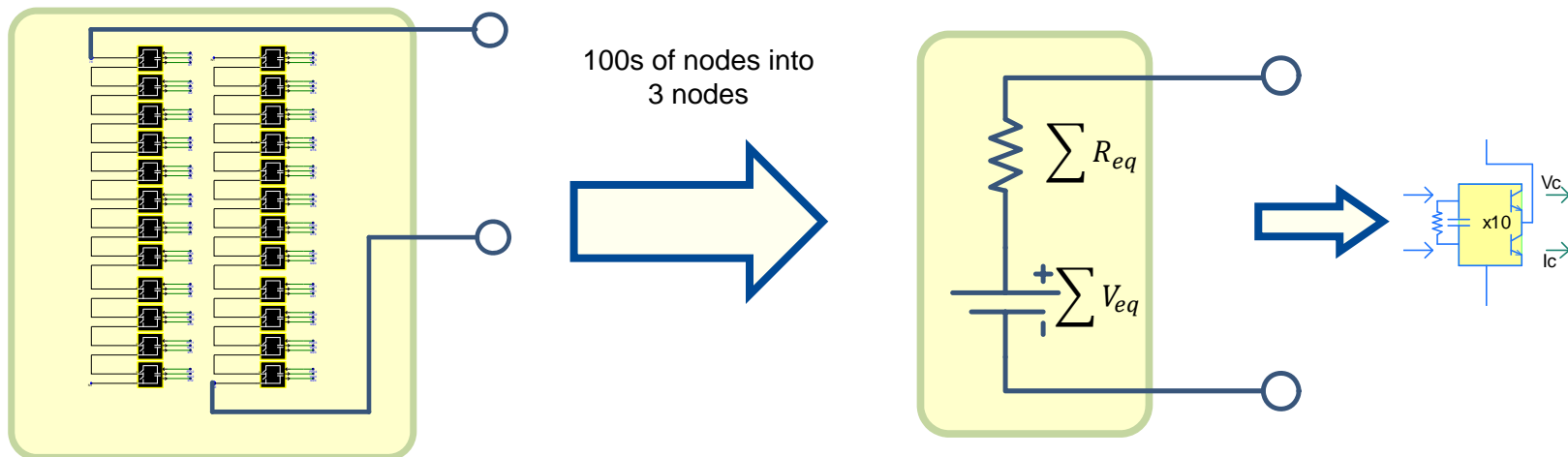
$$V_{eq} = \frac{R_1}{R_1 + R_2 + R_C} V_C$$



- This type of model is identified in CIGRE WB B4-57 as model Type-4
- This model is good for system wide studies and for most DC fault simulations

Start-up sequence

Converter 1: Grid-connected mode → Controls V_{dc} and Q (or V_{ac})

Converter 2: Grid-connected mode → Controls P and Q (or V_{ac}) – in black start mode

Converter 1


- Energize transformer & Pre-charge
- Bypass pre-insertion resistor
- Deblock converter 1
- Regulate V_{dc}




Converter 2

After V_{dc} is regulated:

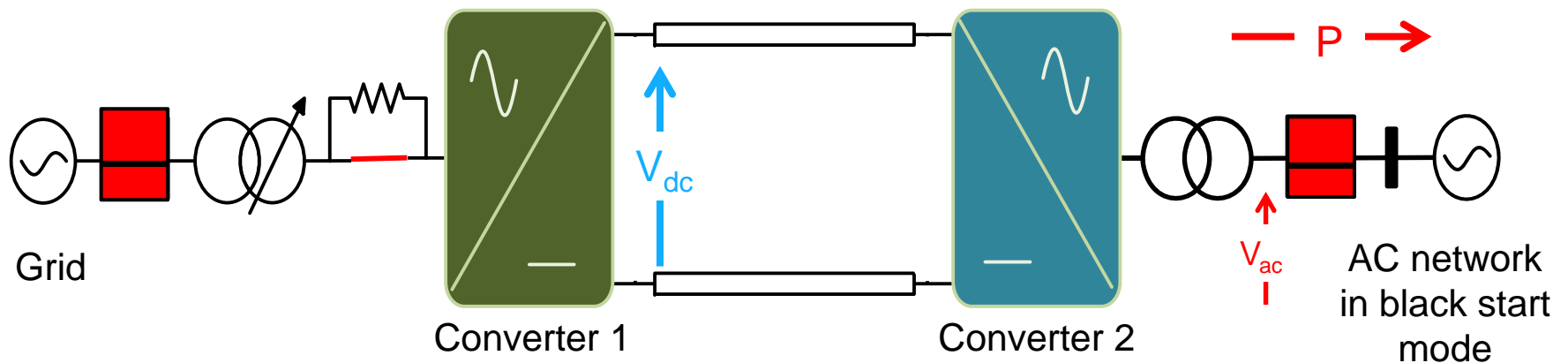- Deblock converter 2
- Regulate V_{ac}
- Ramp-up power transfer




Start-up sequence

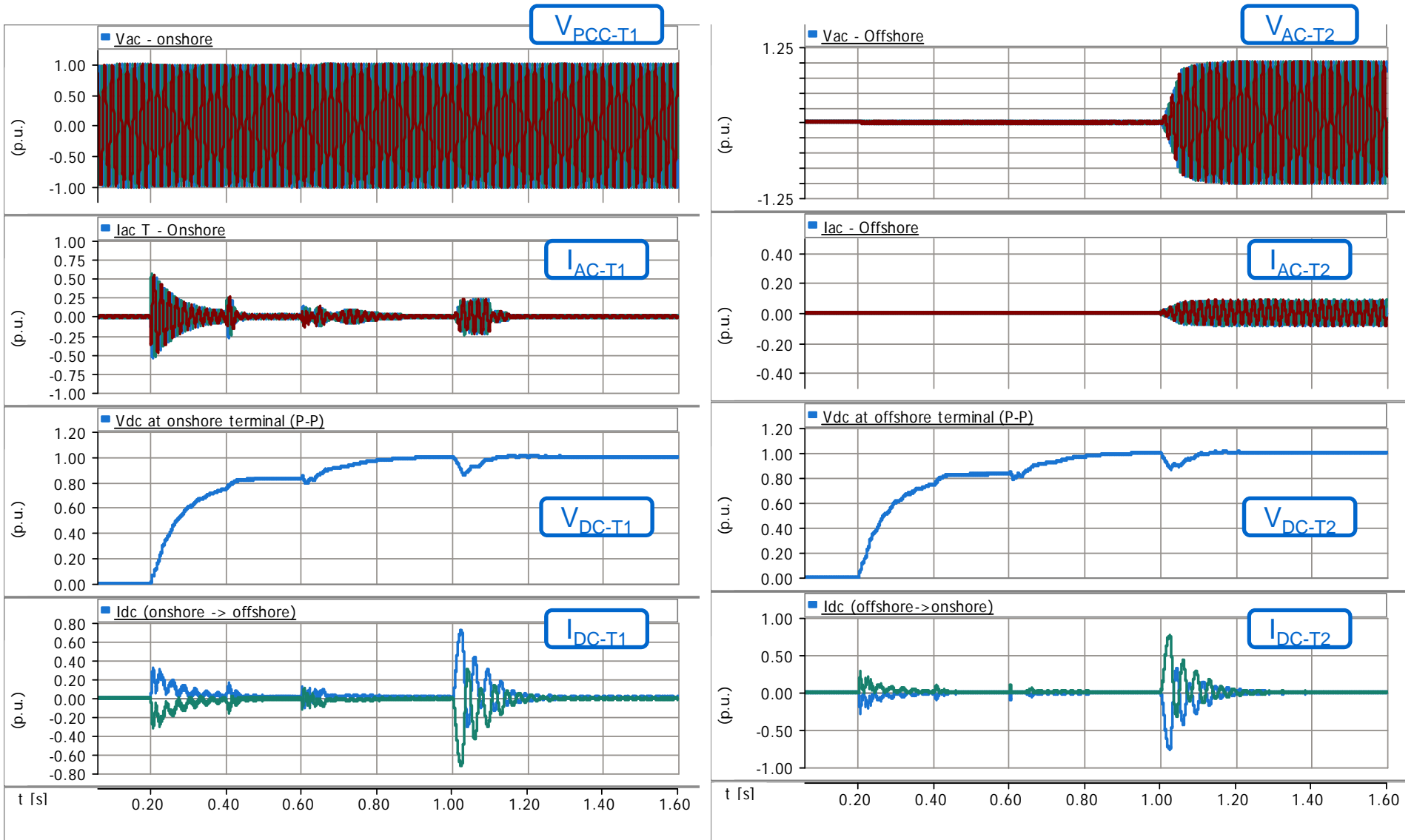

Half-bridge DC faults performance

- Sustained DC faults (unlike LCC)

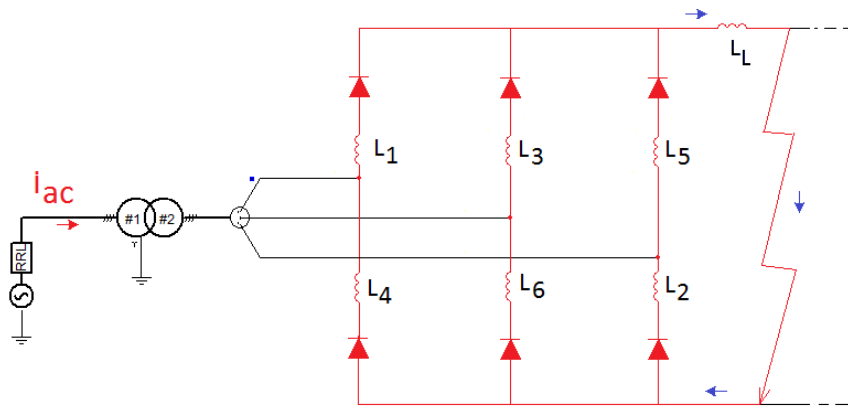


**Applies to conventional
2-Level VSC and
Half-bridge MMC**

- Most systems (except one) use cables:
 - No need for fast re-energization
 - Cables experience low occurrence of faults
 - Fault clearing by opening AC breaker


Half-bridge DC faults performance

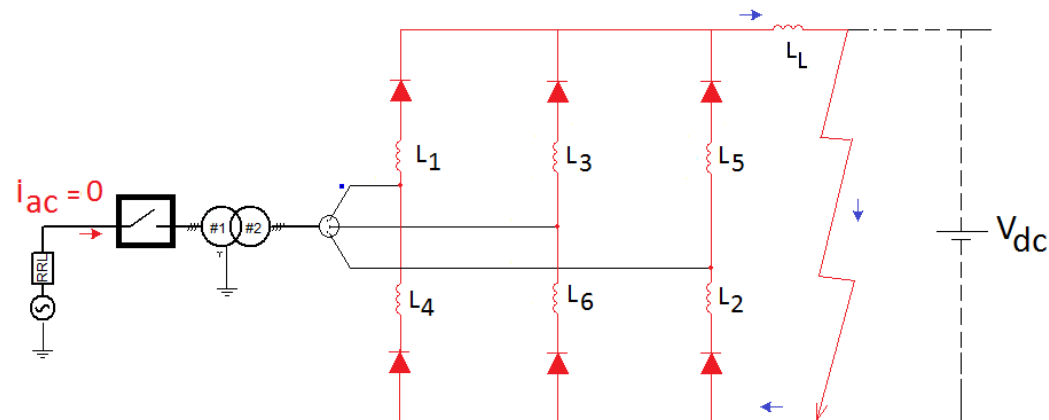- Most systems use cables:
 - No need for fast re-energization
 - Cables experience low occurrence of faults
 - Fault clearing by opening AC breaker




DC faults in VSC systems with Overhead Lines (OHL)

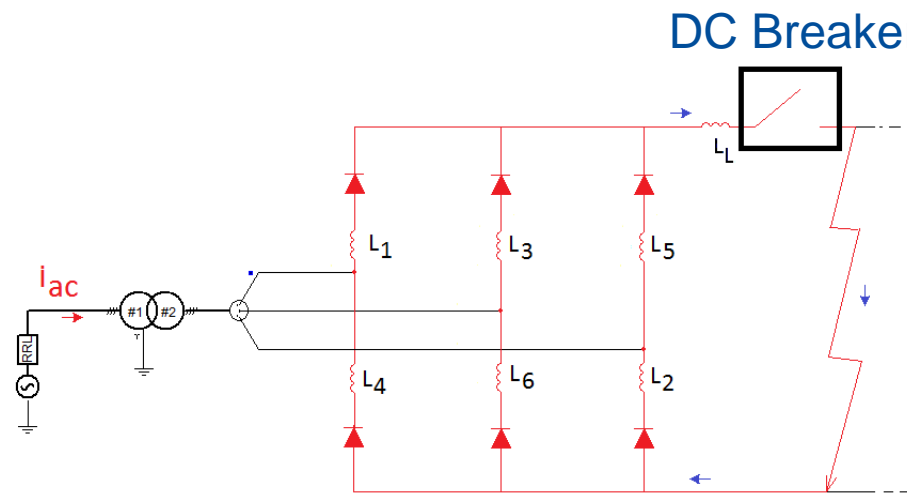- High fault event frequency with OHL
- Need fast re-energization (re-closing) (400-500 ms) to prevent AC system movement
- DC breakers are required in order to achieve fast re-energization of DC system




DC-Breakers

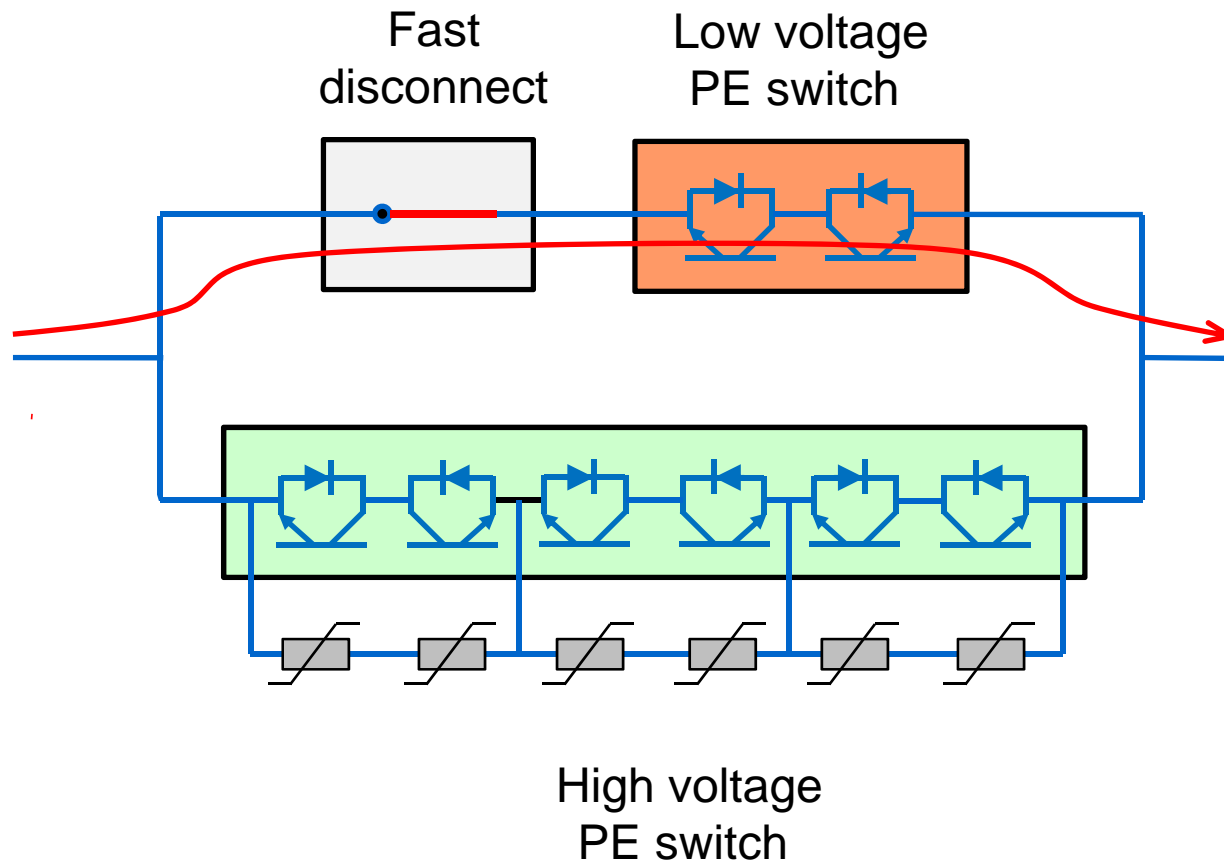

1. Overcurrent or DC fault under voltage front detected

Half-bridge DC faults performance


DC-Breakers

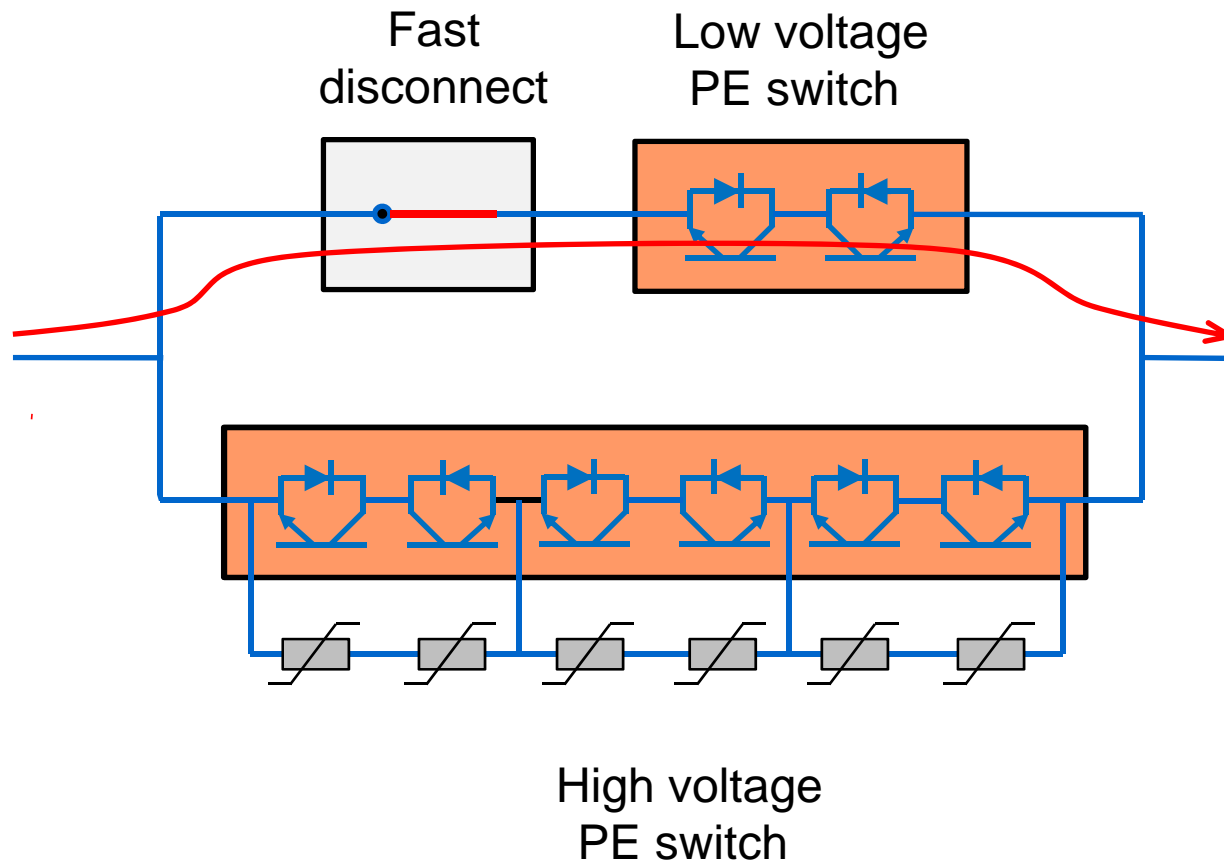

1. Overcurrent or DC fault under voltage front detected
2. De-block HV PE switch

Half-bridge DC faults performance


DC-Breakers

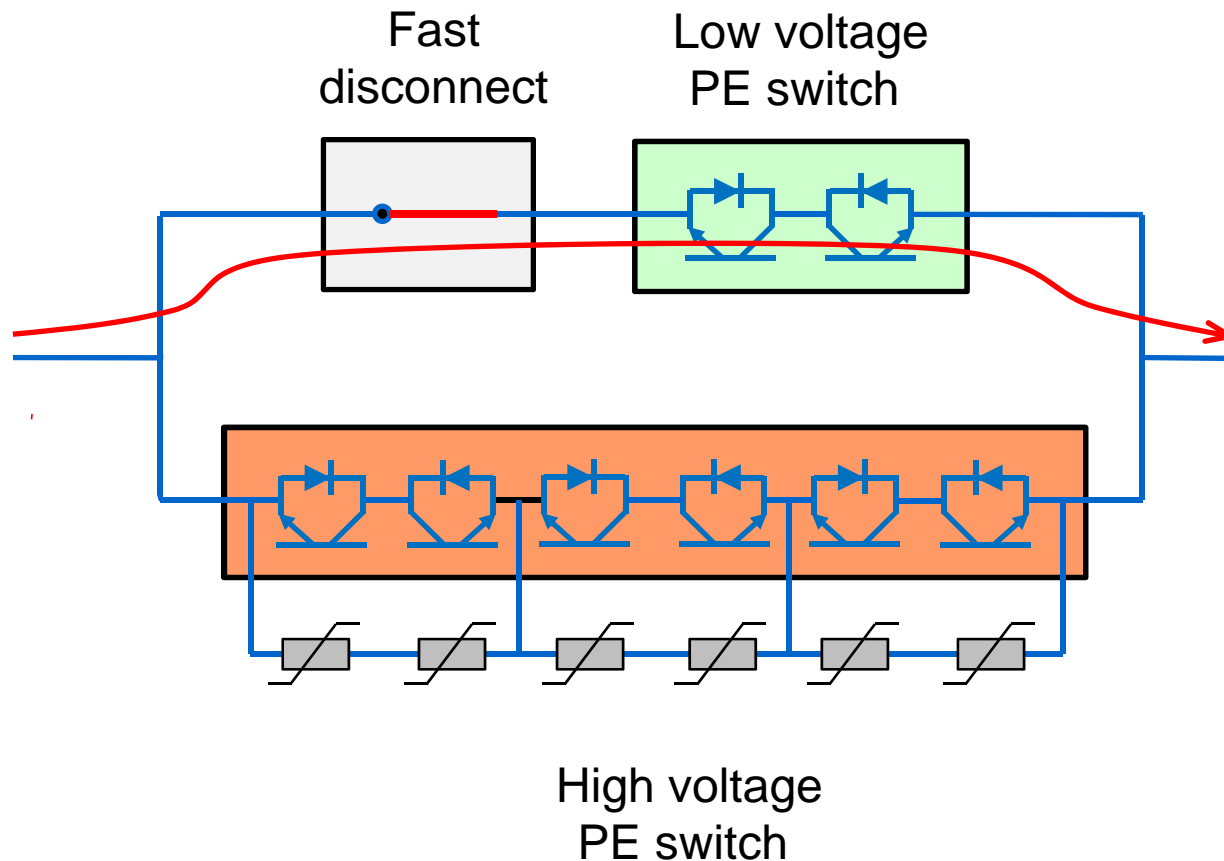

1. Overcurrent or DC fault under voltage front detected
2. De-block HV PE switch
3. Open LV PE switch

Half-bridge DC faults performance


DC-Breakers

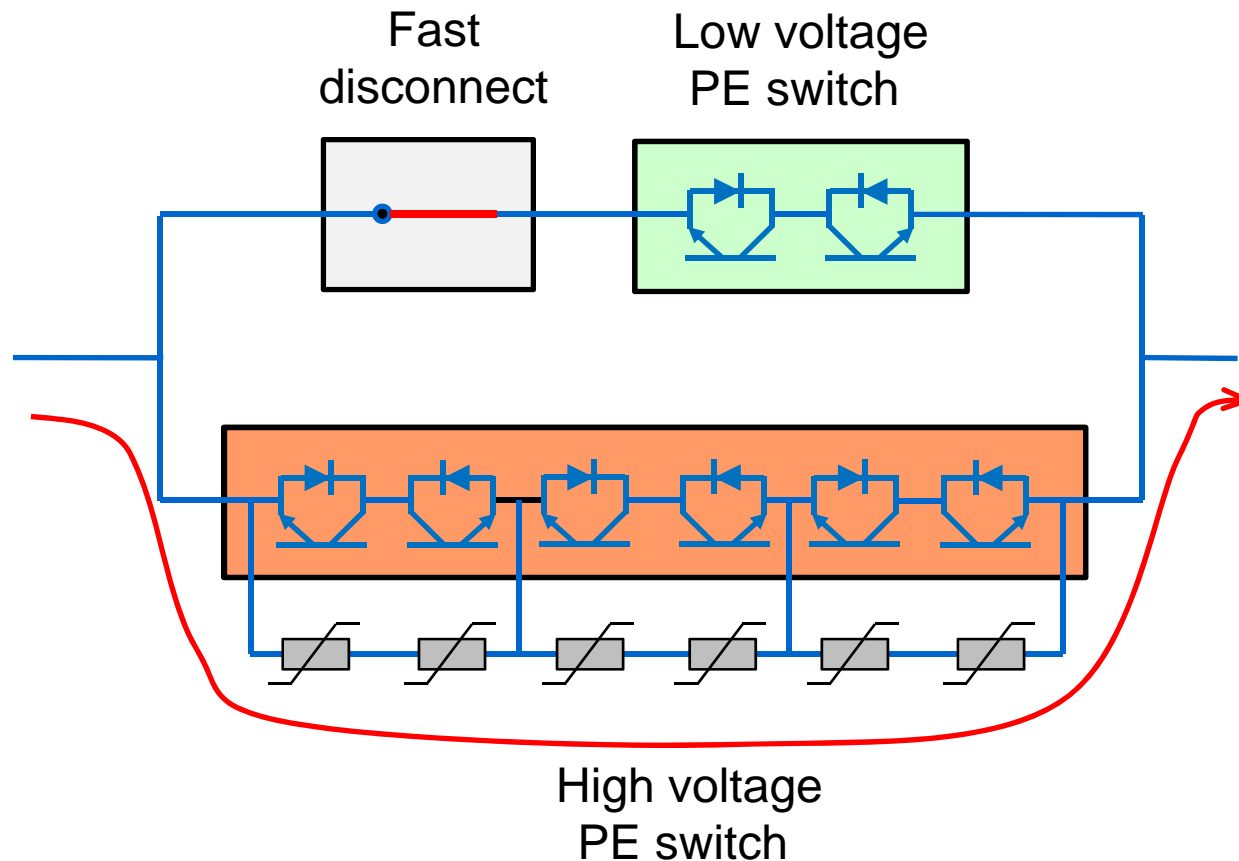

1. Overcurrent or DC fault under voltage front detected
2. De-block HV PE switch
3. Open LV PE switch
4. Current transferred to HV PE switch

Half-bridge DC faults performance


DC-Breakers

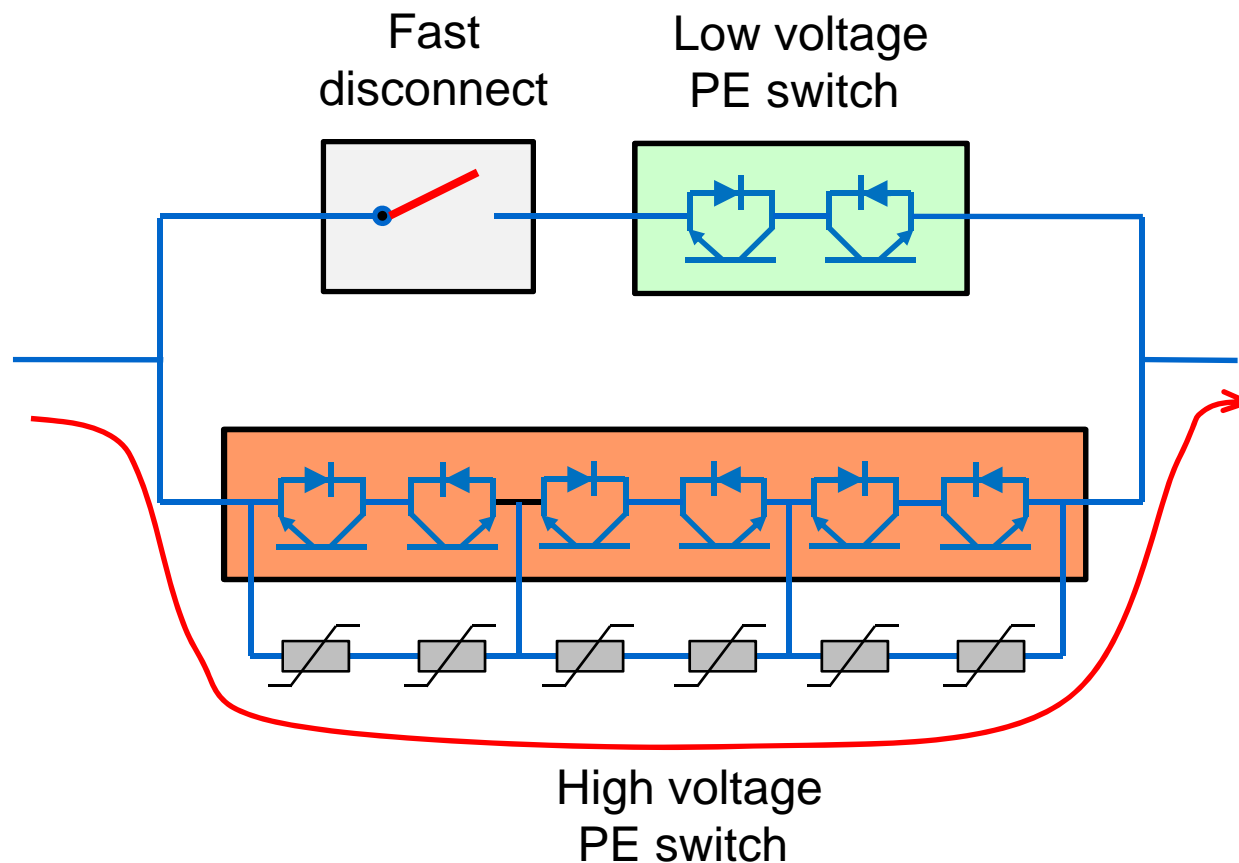

1. Overcurrent or DC fault under voltage front detected
2. De-block HV PE switch
3. Open LV PE switch
4. Current transferred to HV PE switch
5. Open fast disconnect


Half-bridge DC faults performance

DC-Breakers

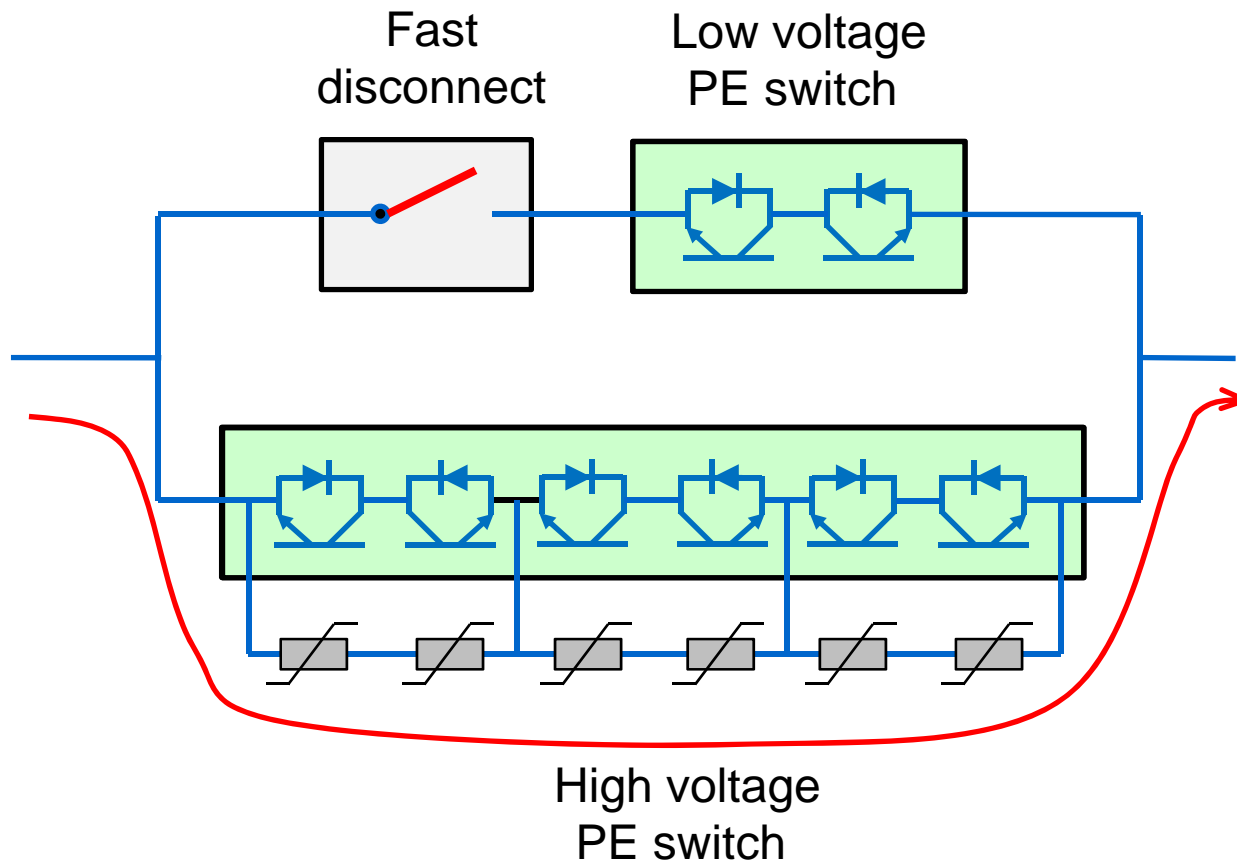


1. Overcurrent or DC fault under voltage front detected
2. De-block HV PE switch
3. Open LV PE switch
4. Current transferred to HV PE switch
5. Open fast disconnect
6. Open HV PE switch

DC-Breakers

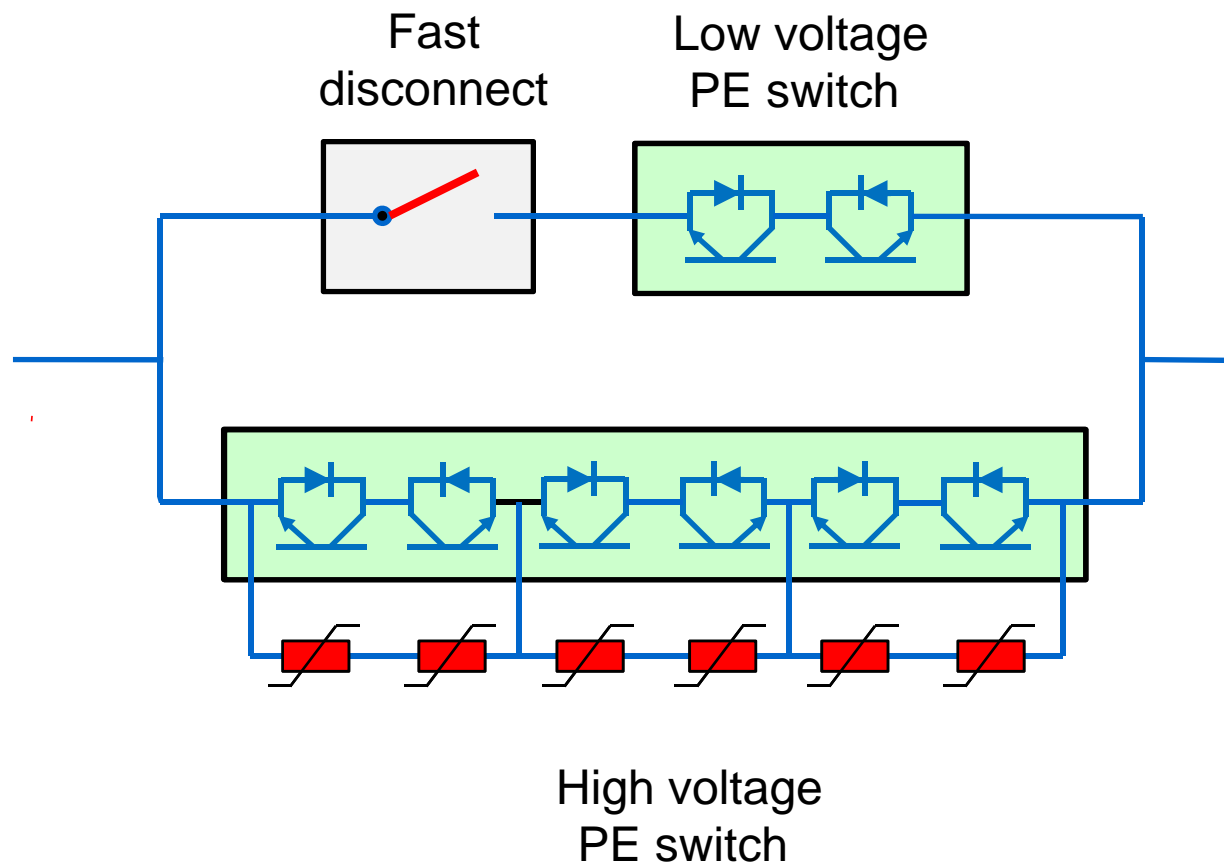

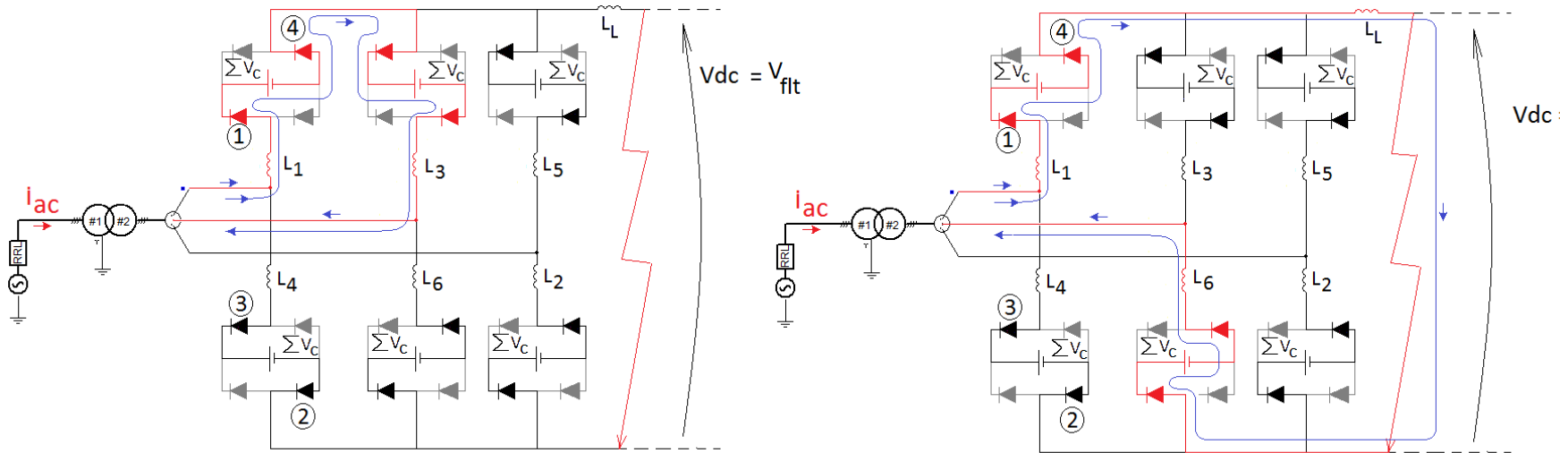1. Overcurrent or DC fault under voltage front detected
2. De-block HV PE switch
3. Open LV PE switch
4. Current transferred to HV PE switch
5. Open fast disconnect
6. Open HV PE switch
7. DC current extinguished & energy dissipated in arresters

Fault clearance in H-bridge VSC systems (by blocking)



$$|i_{AC}| \begin{cases} > 0 & \text{if } v_{AC \ l-l} \geq 2 \sum_i k_i v_c \\ = 0 & \text{otherwise} \end{cases}$$


- Therefore $i_{ac}=0$ after blocking since

$$V_{AC \ L-L \ pk} = m \sqrt{3} V_{dc} \quad \longrightarrow \quad m \sqrt{3} V_{dc} \not\geq 2 V_{dc}$$


$$\sum v_c = V_{dc}$$

Simulation of DC faults in a two-terminal system

System description

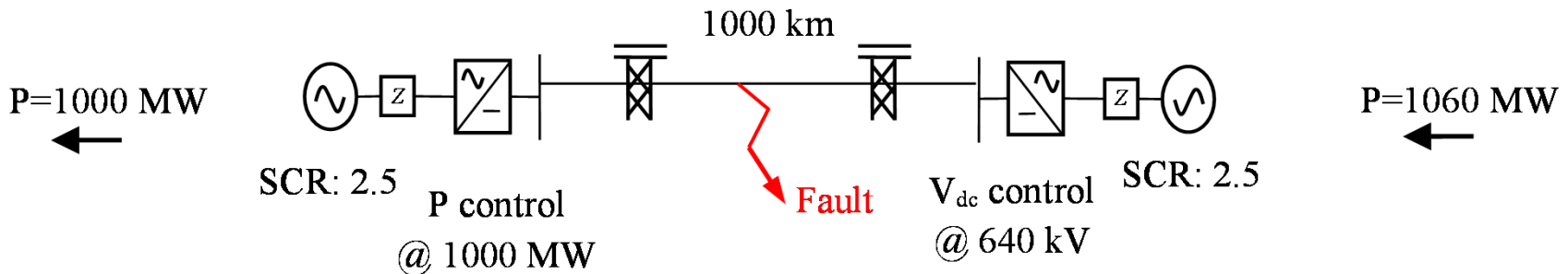

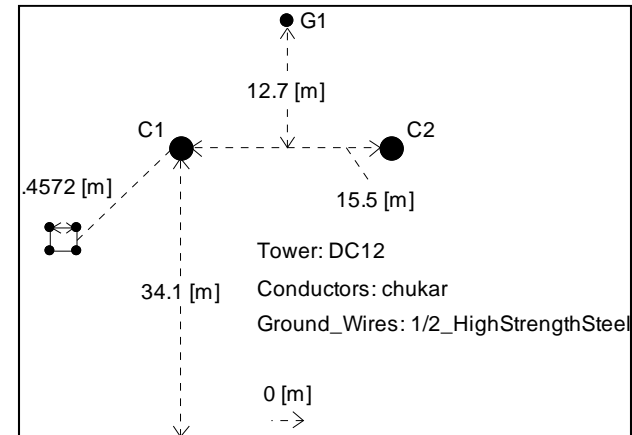
- T1: P control
- T2: V_{dc} control
- T1 & T2 in V_{ac} control



TL Freq. dependent model

Simulation of DC faults in a two-terminal system

DC Faults applied

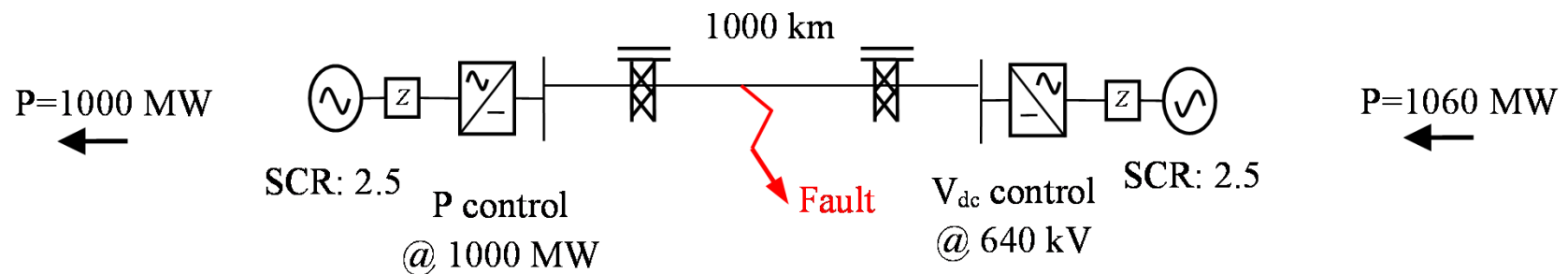


- At close and remote terminals
- Middle of the line
- Low impedance faults (0.1 ohm)

DC Faults detection

- Valve overcurrent (2.7 kA level)
- DC voltage drop (40% of diode rectifier voltage)

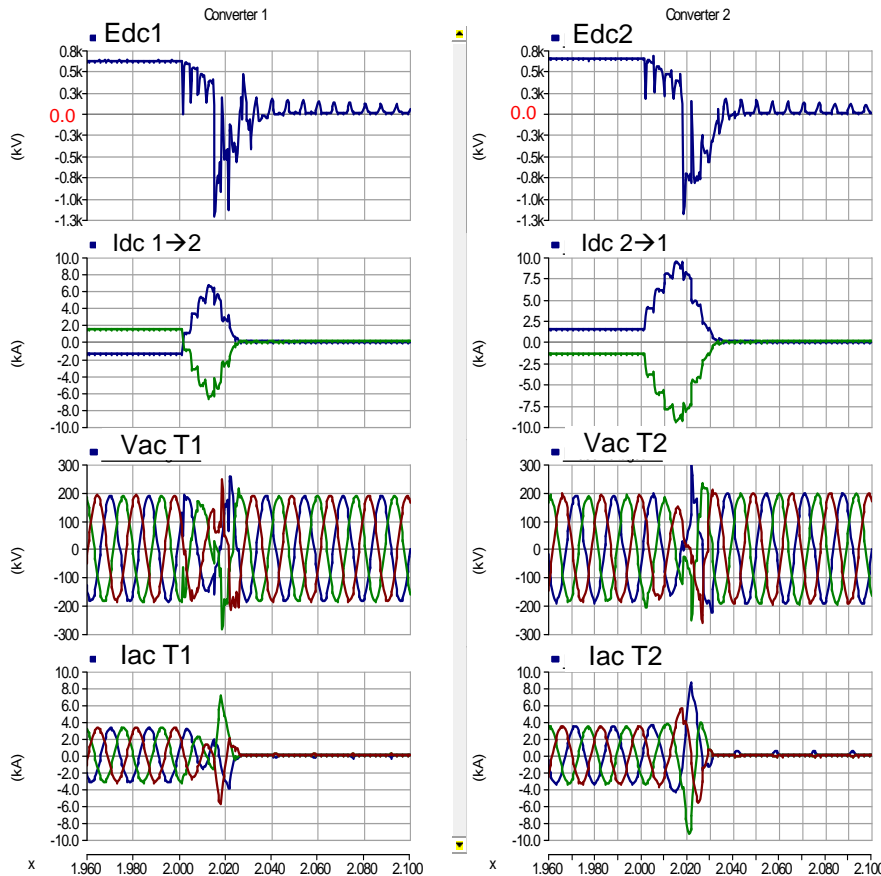Simulation of DC faults in a two-terminal system



- The total time to restore 90% power was 450ms
- Including 200 ms de-ionization time



Three-terminal system: Demonstration setup

- Starting with the two-terminal system from CIGRE B4-57
- If time allows

Questions

- Please e-mail PSCAD Support at

support@pscad.com